
Firefly

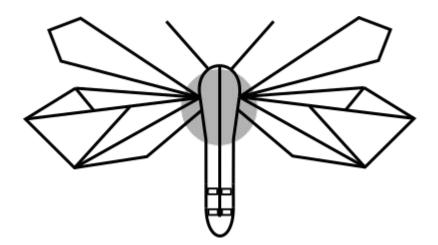
Engineer's approach to creating a dead-simple freeform circuit.









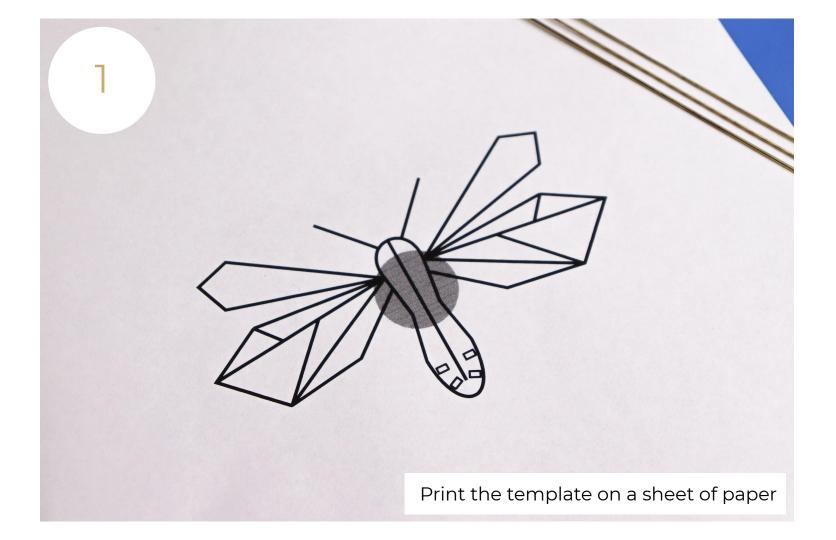
Vector template available on Hackaday workshop site for download







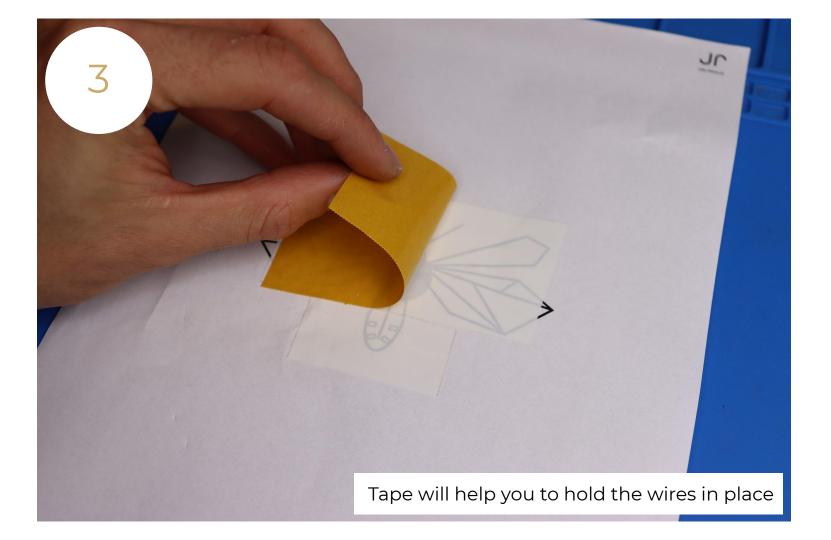


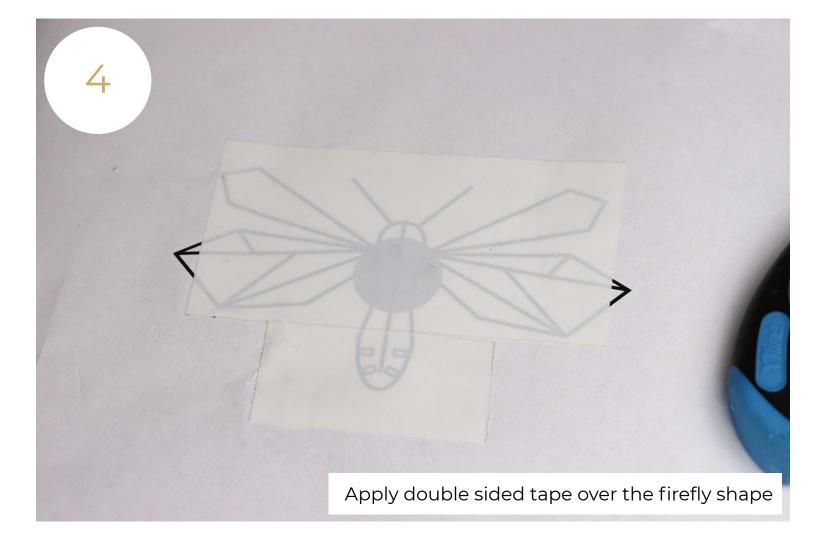


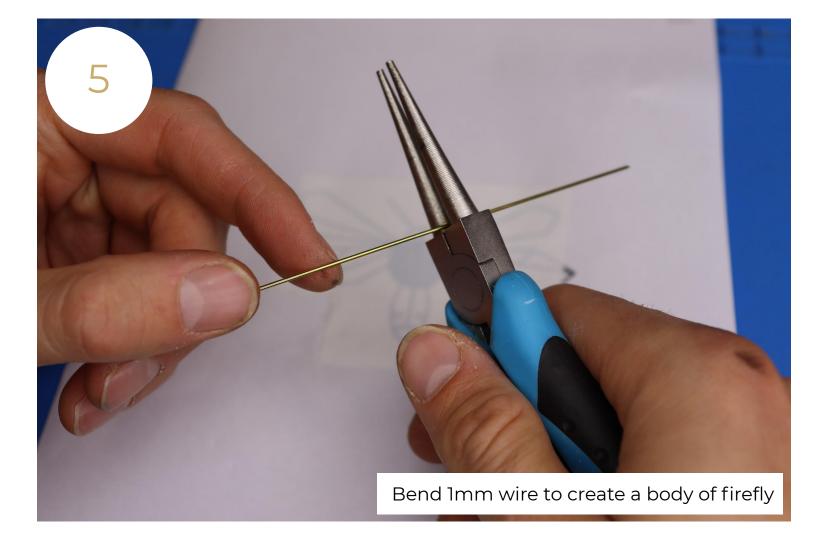


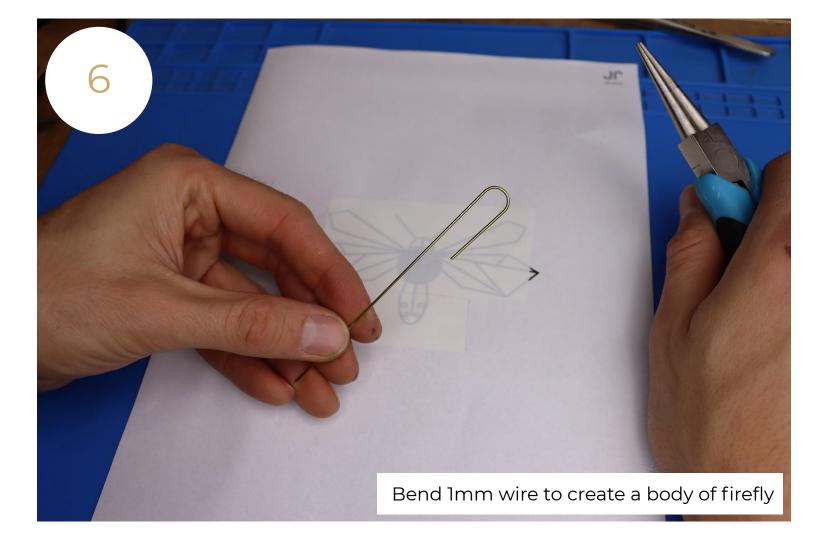

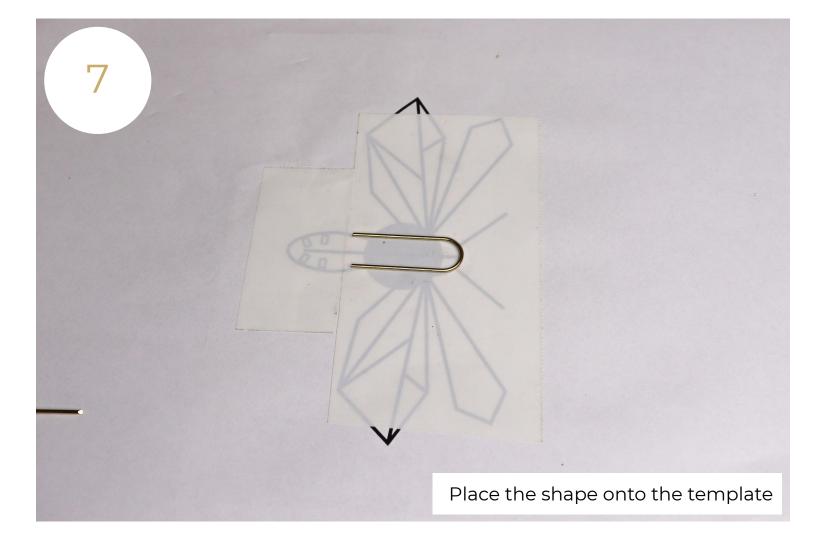


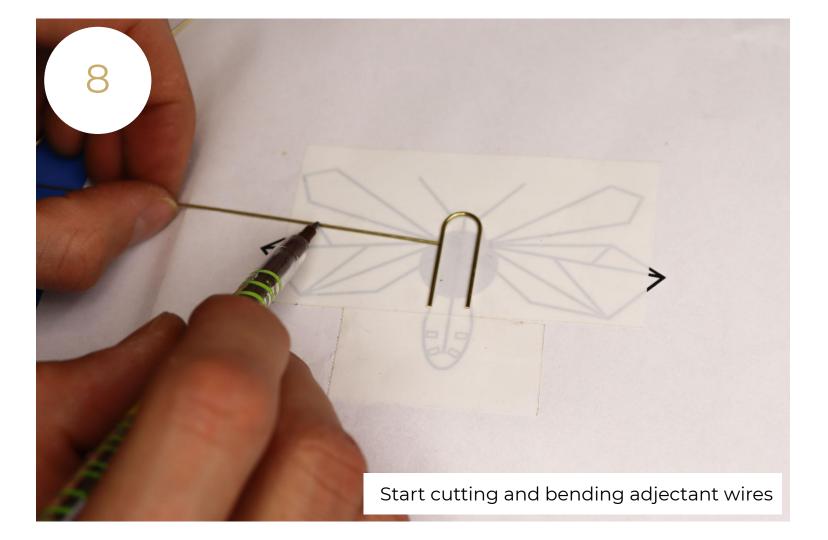


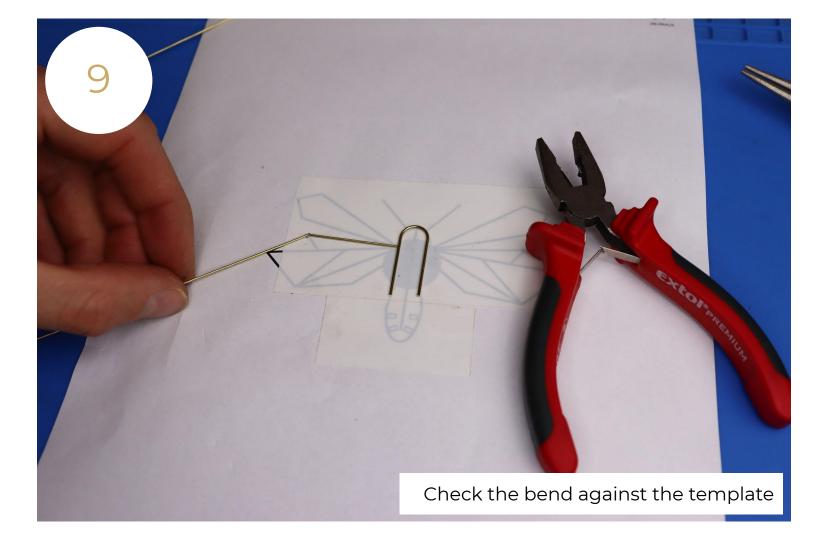


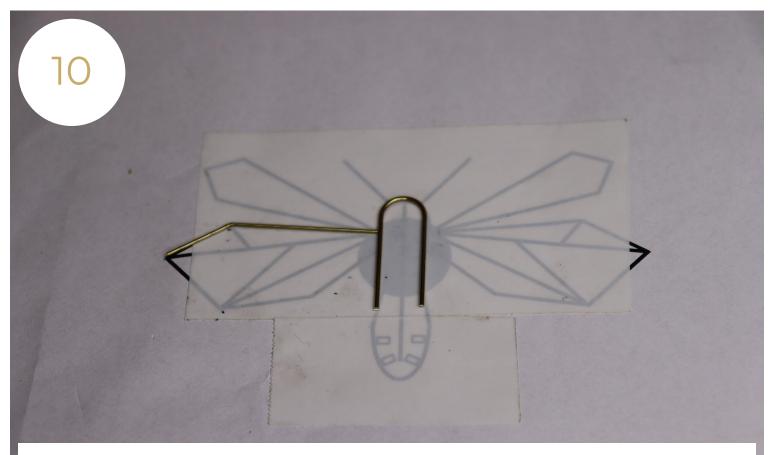


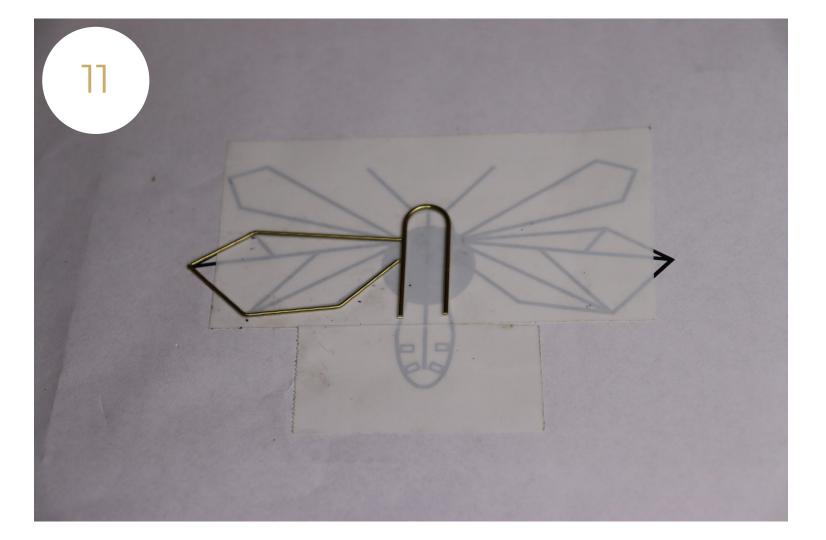
Bends over 90° are hard to make to look nice. So I will cut the wire in joint and continue with new piece.




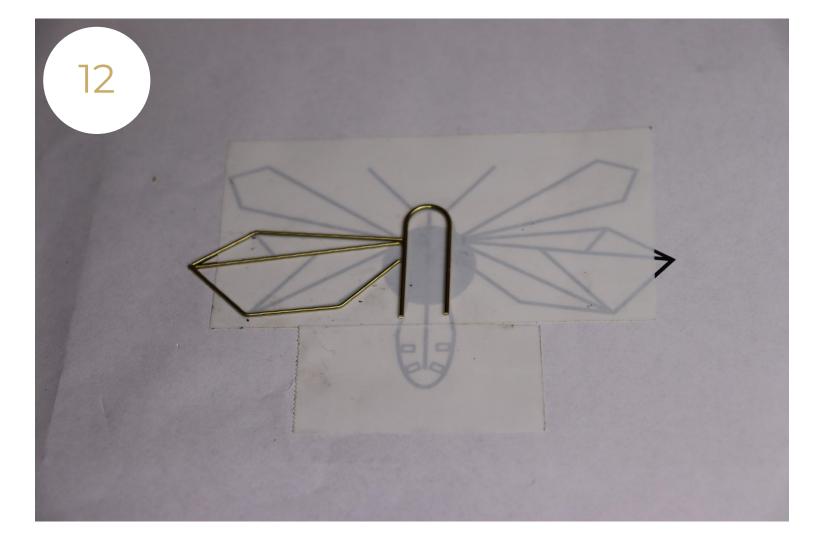

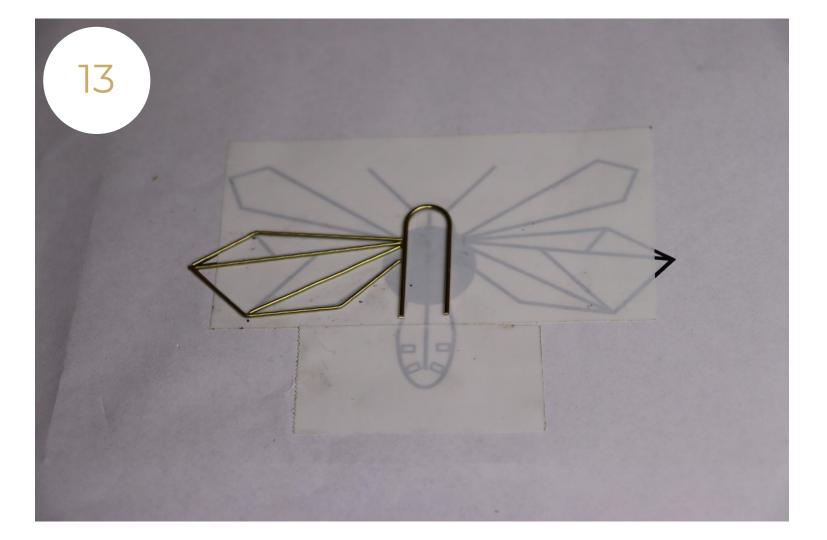


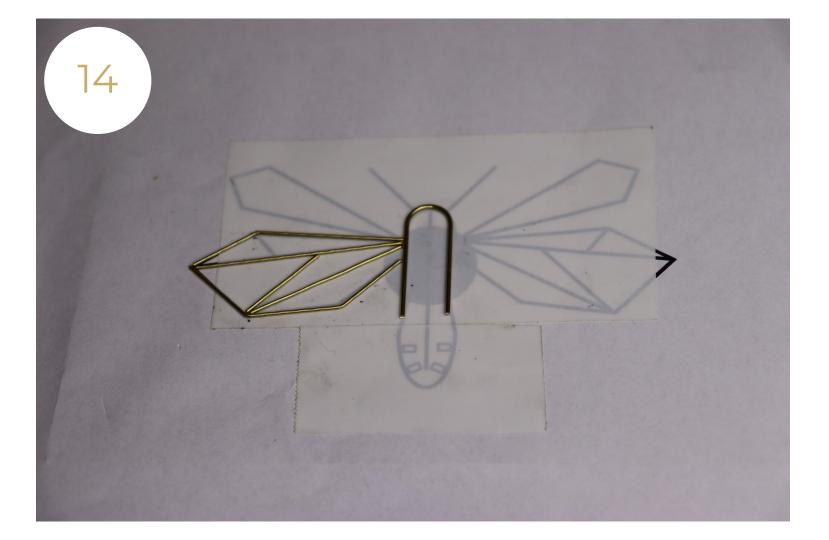


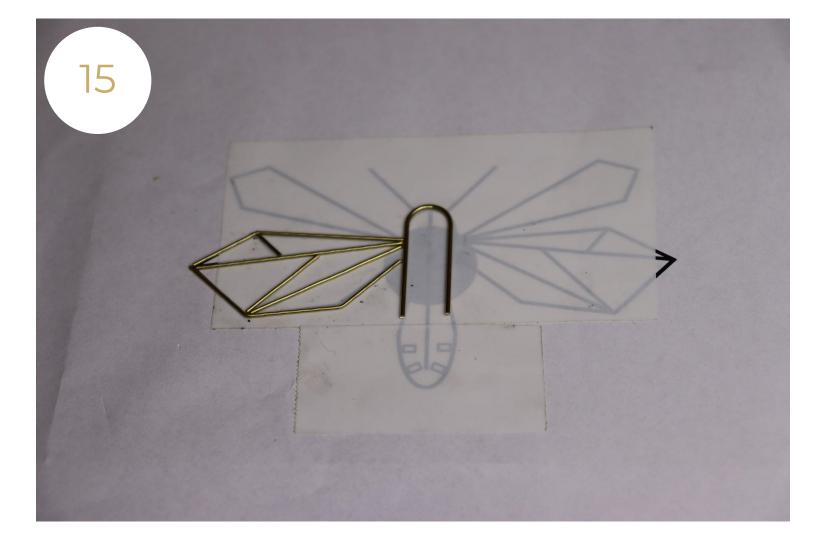


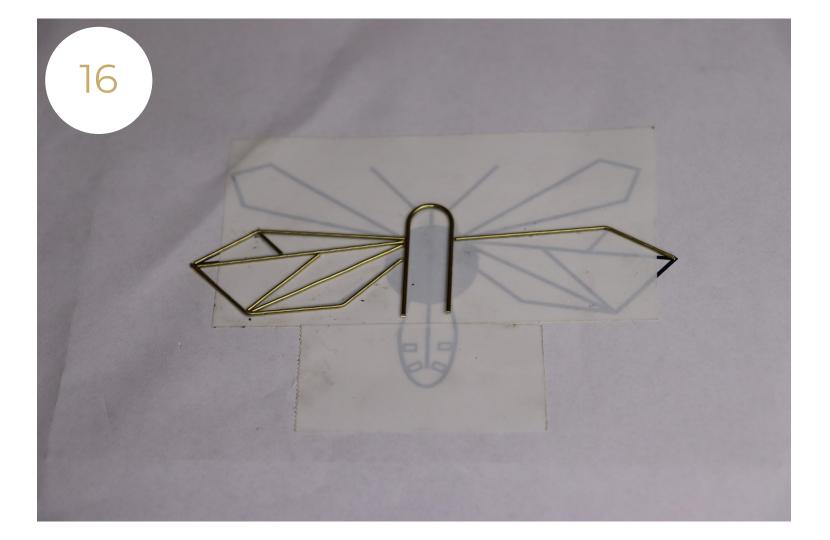





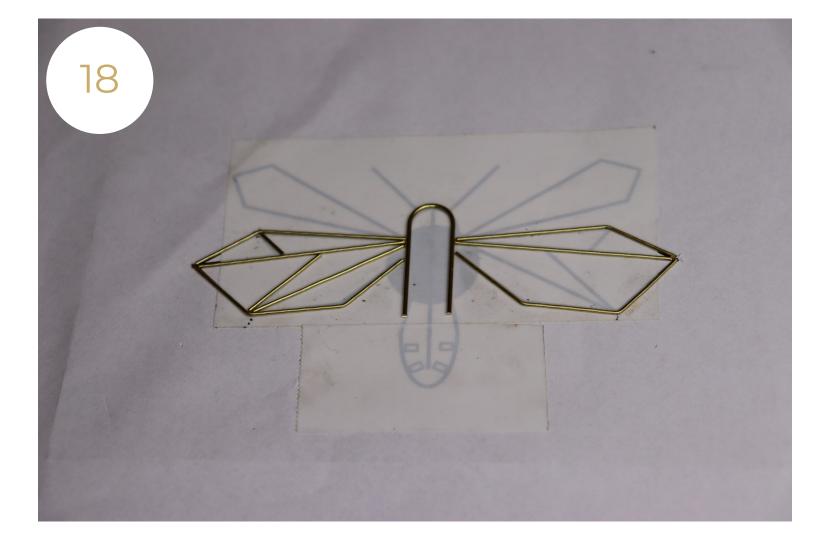


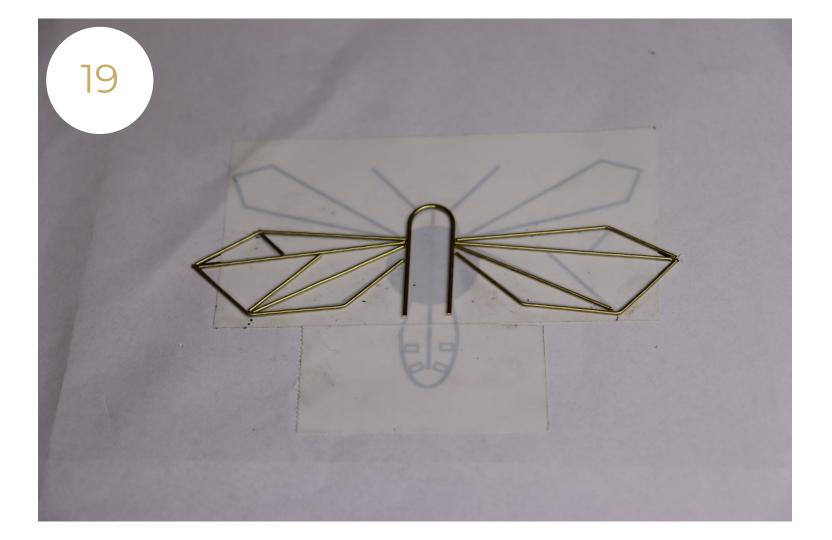

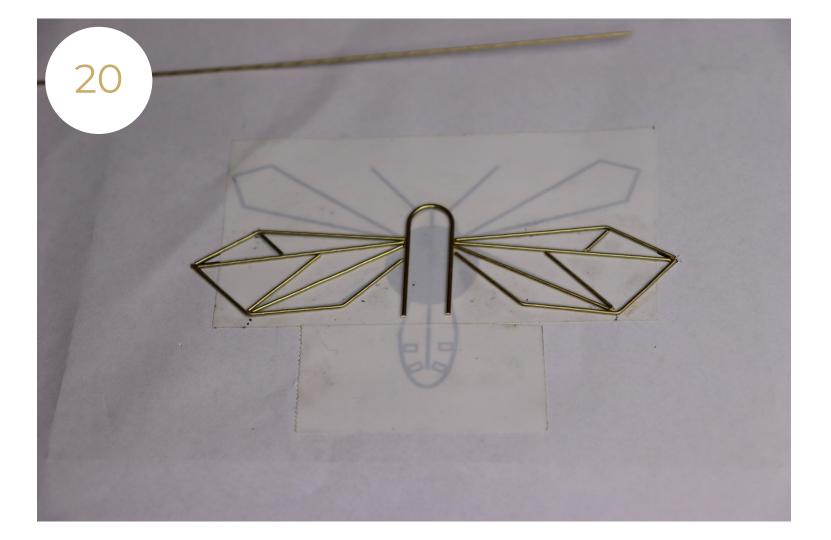

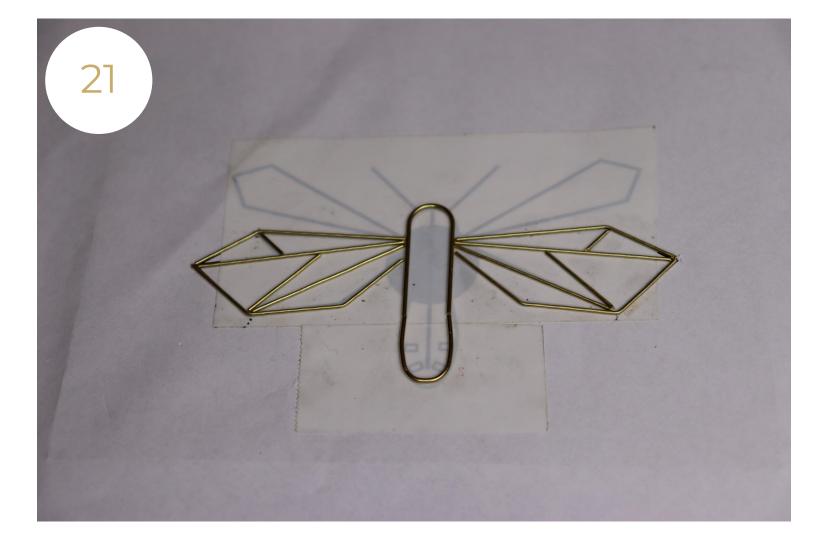

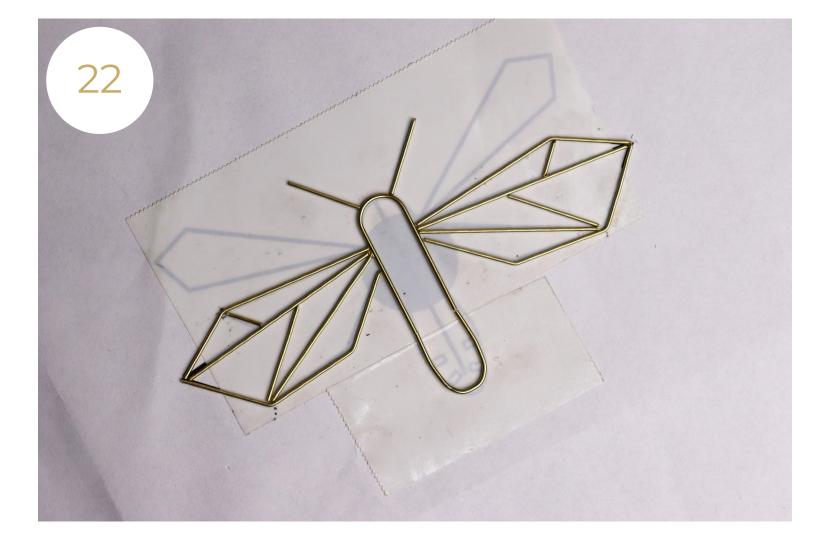

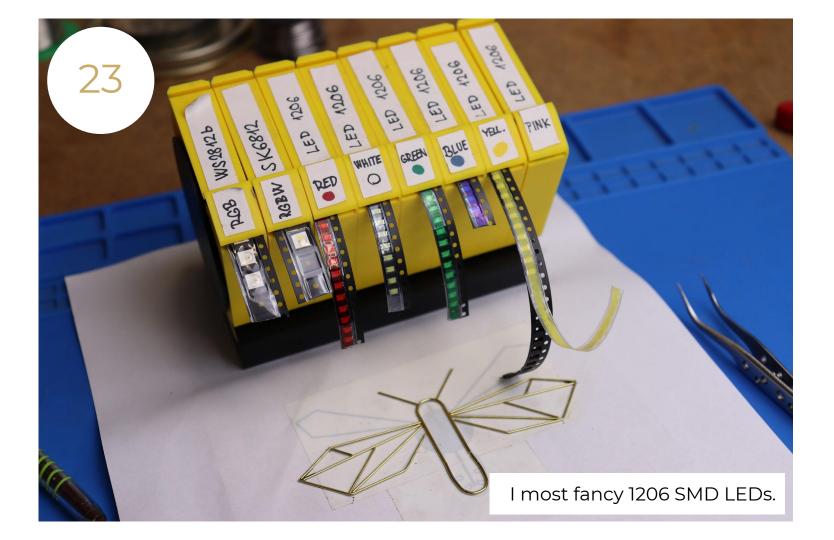



SMD LEDs. They have two leads. Arrows indicates the current flow.

