



GLOW BAG




WEARABLE TECH PROJECT #2

Liven up an old bag or sew a new bag with decorations and light up electronics. The lights come on when the bag is shut!

Make sure the tape makes a good connection with the gold pads on the LEDs. Sandwich the LED pad between two layers of conductive tape if reversing the LEDs to shine through the fabric from the inside of the bag.

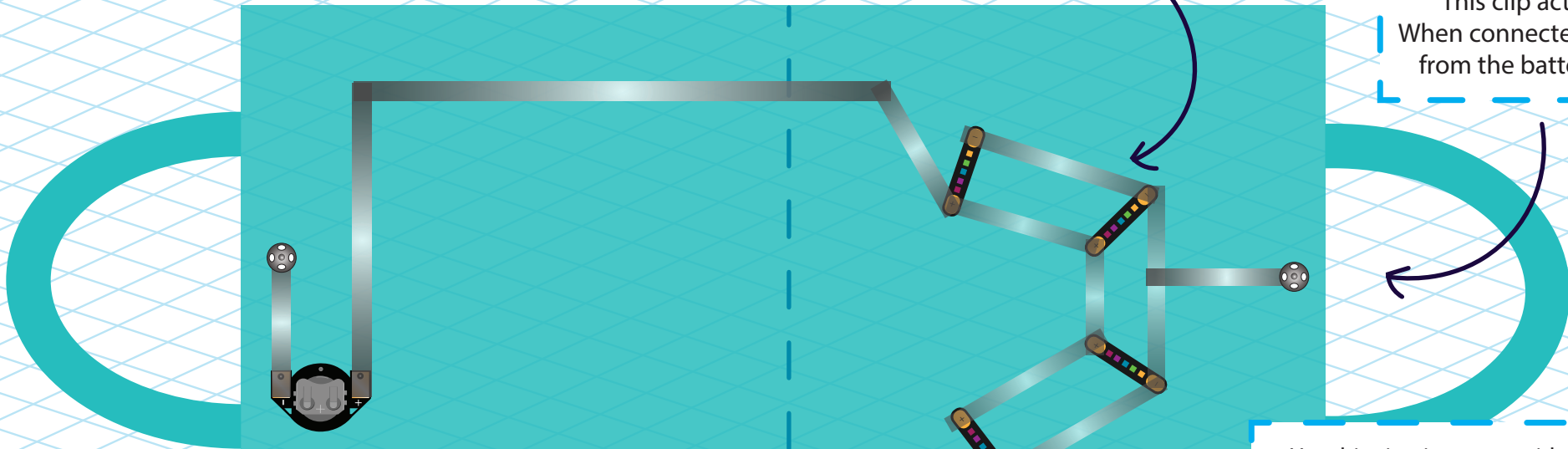This clip acts as a switch. When connected, it brings power from the battery to the lights!



Use this circuit pattern either on the inside or outside of the bag. Use a layer of fabric over the top to protect the circuit if on the inside of the bag. Consider machine sewing to secure your circuit in place. Conductive tape will still function if painted during decoration.



Decorate the front with a rainbow, flower or other design of your choice to finish off your project.

Find more projects and ideas at bit.ly/3pN5qk9

