



Fig. 1. Complete circuit for the 6809 Nanocomp. Resistors R4 to R10 have been reduced to 120Ω for a brighter display, and the 74LS00 has been omitted. The simple 5V power supply used with the original design can also be used for the 6809 version.