

Pin 2 is pulled high with a current limiting resistor of 220 Ohms. When SW1 is pressed pin 2 is pulled to ground causing output to go high (pin 3).


Pin 4 (Reset) is connected to Vcc to prevent accidentally resets.

Pin 5 (CV/Control) is grounded with a capacitor so that it does not consume much power and does not change the default operation of the 555 timer.

This pin controls the threshold and trigger voltages and it is set to $2/3V_{dd}$. The capacitor will help maintain this voltage consistently.

R2 and C2 for our timing circuit. When pin 2 gets pulled to ground DIS becomes an open drain (not connected to Vcc or GND) which allows C2 to charge through R2. Once the threshold (pin 6) reaches the threshold voltage output (pin 3) will go low and the discharge pin will also go low causing the capacitor to quickly discharge. On page 15 of this datasheet, <https://www.ti.com/lit/ds/symlink/tlc555.pdf>, we see the capacitor will take approximately $(1.1)(C2)(R2)$ to reach the threshold voltage. In this project a large resistor is chosen in conjunction with a medium value capacitor to create a 36s output time.

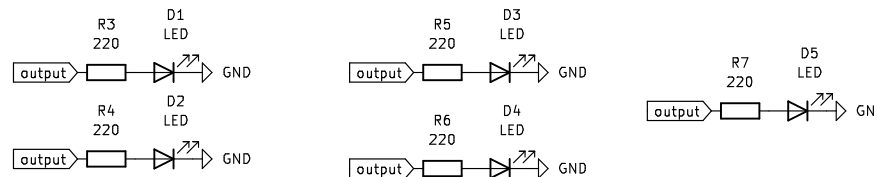$t = 1.1 * R * C = 1.1 * (10\text{Mohm}) * (3.3\mu\text{F}) = 36.3\text{s}$
 Will not be exactly that since the capacitor is rated to within 20% of its value and the resistor is within 5% of its value.
 A more accurate resistor and capacitor would make a more accurate timer. The 555 is most definitely the most accurate component here.



Let's figure the approximate LED current.
 $V_{cc} = 6V$ (will be a bit less)
 $V_{pld} =$ forward voltage of the purple LED = 3.2V
 $V_{rled} =$ forward voltage of the red LED = 2V
 $V_{oled} =$ forward voltage of the orange LED = 2V
 $R = 220\text{ Ohm}$

$I_{rled} = I_{oled}$
 $V = V_{cc} - V_{rled} = IR$
 $I_{rled} = 4V / 220\text{ Ohm} = 18\text{mA}$

$I_{pld} = 13\text{ mA}$

There may be rounding errors in these calculations but they should be fairly close.
 This means that the total current consumption is just under 50mA when turned on.

We have two CR2032 batteries which have approximately 235mAh, <https://data.energizer.com/pdfs/cr2032.pdf>, so that is 470mAh. Our little device should be able to last 9 hours on (1080 cycles).
 This will vary based on how long you leave it not on since a small amount of current will be used when off. Where do you think that current is?

Let's figure the off current.
 The 10M Ohm resistor will have a current draw.
 $V_{cc} = IR \rightarrow 6V = I (10M\text{ Ohm})$
 $\rightarrow I = 6V / (10M\text{ Ohm}) = 0.6\mu\text{A}$ (micro-amps!)

Not very much there!

On page one of the data sheet we see $P = 1\text{mW}$ at $V_{dd} = 5V$
 let's figure out the current consumption:
 $P = VI \rightarrow I = P/V \rightarrow I = 1\text{mW} / 5V = 0.2\text{mA}$.

So that is more significant!

Plus our batteries discharge about 1% a year by themselves (see energizier doc).

In one year our 555 timer will use approximately 1752mA, so our batteries would be drained.

Let's figure how long it will last approximately
 $I = 0.2\text{mA}$
 $P_{batt} = 470\text{mAh} = I * (\text{time in hours})$
 $\rightarrow \text{time} = 470\text{mAh} / 0.2\text{mA} = 2350\text{ hours} = 98\text{ days}$
 So approximately 3 months!

Should be enough for easter season.