

retro 1 design/learning log


1. Setup Circuit like here (except don't use SO pin):
<http://www.grappendorf.net/projects/6502-home-computer/eprom-and-a-first-program>
2. Add a 3.3k resistor between BE pin and vcc (this is needed for 65c02)
3. hook up logic analyzer to data pins and check that data is correct ie:
A9,12,4C,00,80 etc...


Code (note I changed fff0 address to 1ff0):

```
00008000 a9 12 4c 00 80 00 00 00 00 00 00 00 00 00 00 00
00008010 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
*
00001ff0 00 00 00 00 00 00 00 00 00 00 00 80 00 80 00 80
00010000
```

What's happening?

When the 65C02 starts up it first will execute whatever code is at the reset vector. Therefore it'll put 1ffc and 1ffd (the reset vector location. Actually the real location seems to be fffc and fffd) out on its address bus. It's up to the glue logic to make sure the rom is setup to respond to this address. The above reset vector points to address 8000 (remember that this is written in little endian so the 80 will be before 00). In this particular circuit, there is no glue logic. We wire up rom oe/ce to ground and we to vcc. This essentially just makes the rom spit out whatever data is on the address bus. Next we will try to add some glue logic.

 

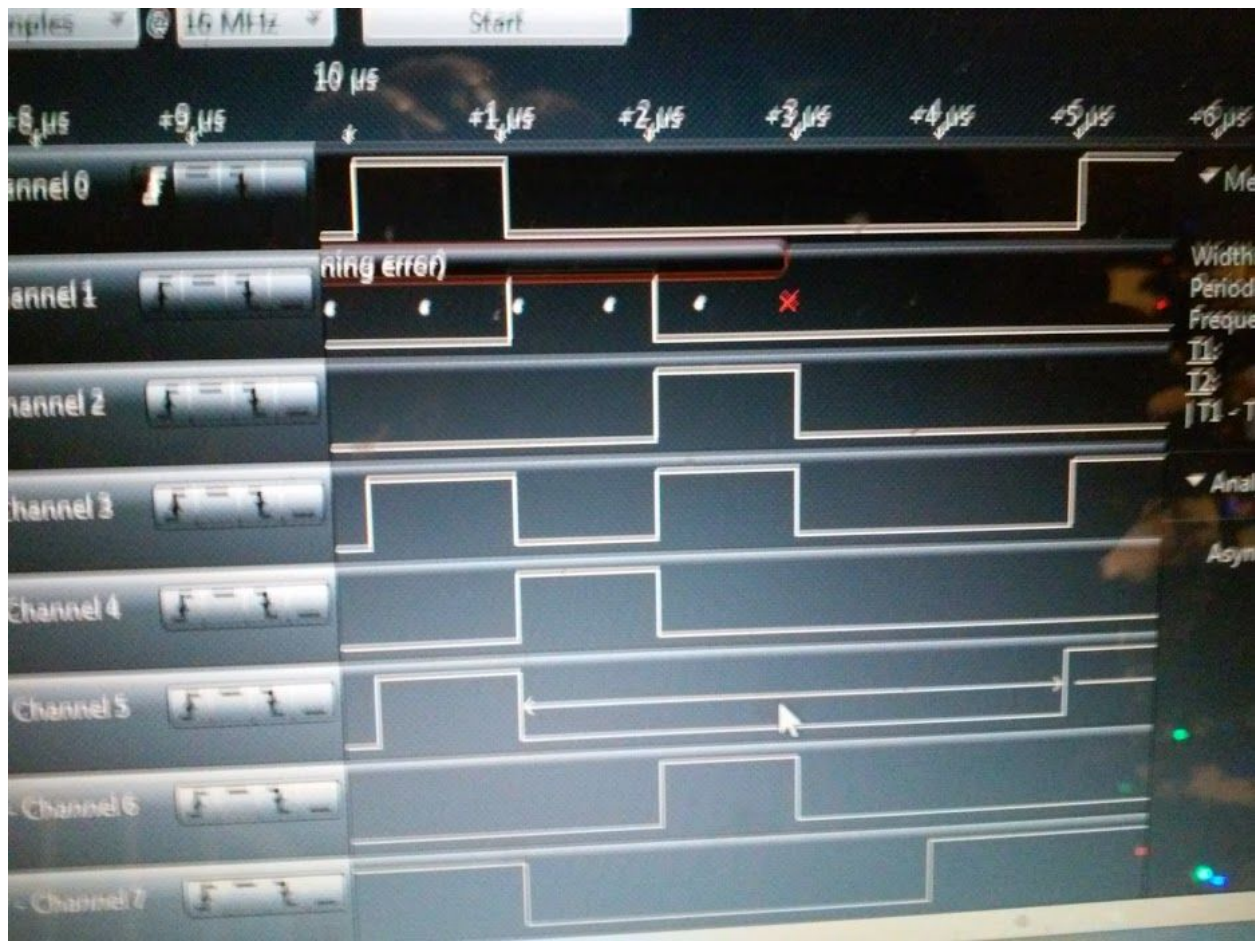

Basic Glue Logic

Keep 65c02 setup as above. Setup via/decoder as explained here
[:http://www.reocities.com/SiliconValley/2072/6502prj1.htm](http://www.reocities.com/SiliconValley/2072/6502prj1.htm).


1. For program, since we're using the AT28C256 ROM, our reset vector is at 7FFC/7FFD. And our code will have to start at address 6000 to work without modifying anything else.
 - a. I figured out reset vector since the cpu will look for the vector at FFFC/FFFD - but since the AT28C256 only has 15 address lines, it won't see the last binary 1. So instead of 1111111111111100(FFFC) the ROM will see 111111111111110(7FFC).
 - b. if our reset vector contains E000, that will translate to address 6000 by the ROM since it will only see the lower 15 address lines (ie instead of 1110000000000000 it sees 1100000000000000)

Better glue logic

keep BE set high as well as RDY, IRQ, and NMI to vcc. Setup 74ls00 for address decoding as shown here:

<http://zx80.netai.net/grant/6502/Simple6502.html>
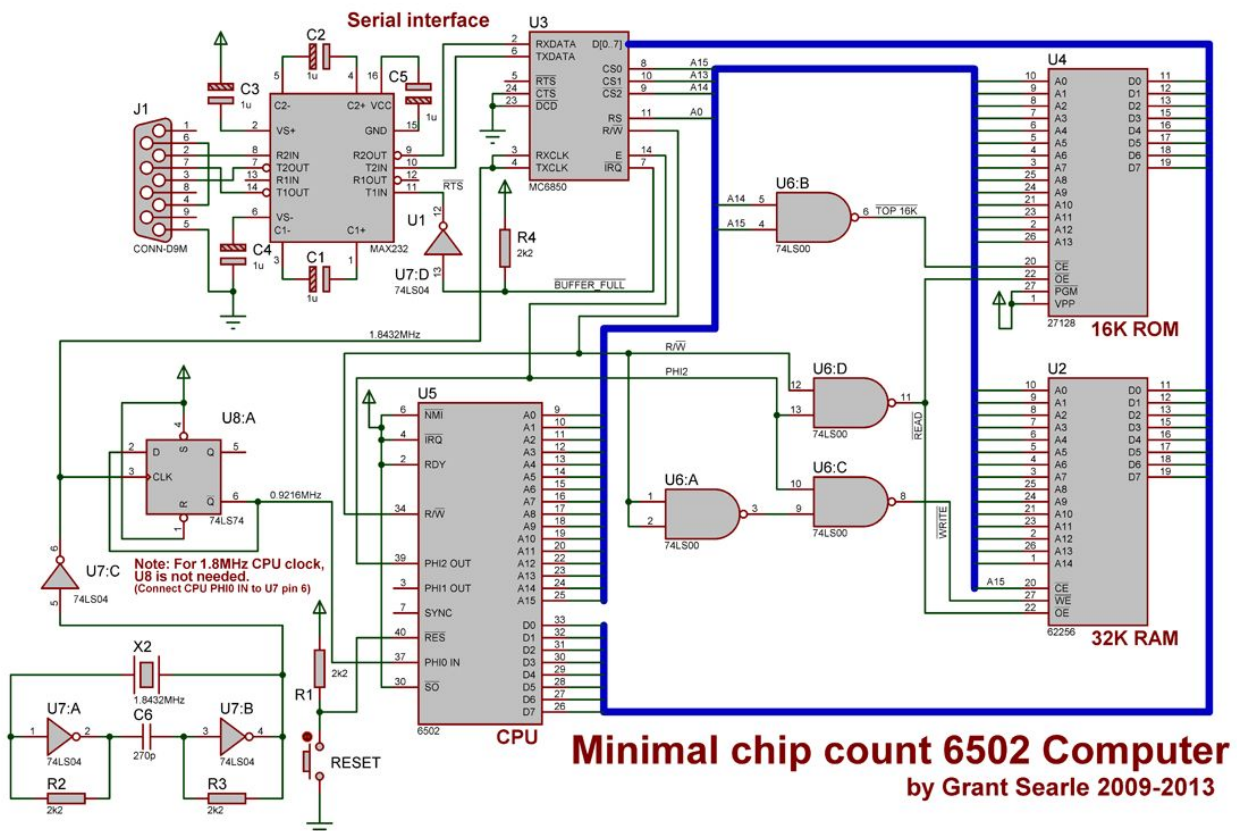
<https://web.archive.org/web/20130816003149/http://searle.hostei.com/grant/6502/Simple6502.html>



This creates the following memory map:

0000-7FFF 32K RAM

8000-9FFF FREE SPACE (8K)

A000-BFFF SERIAL INTERFACE (minimally decoded)

C000-FFFF 16K ROM (BASIC from C000 TO DED3, serial routines FF00 to FFFF, so a large amount of free space suitable for a monitor etc)

As you can see this memory map has the RAM at the beginning of the map, the IO in the middle, and the ROM placed at the end. This is fairly typical of computers built around the 80s. We typically place the ROM at the end of the map because that's the address that the reset

vector will try to access. Having the RAM at the beginning gives us options of having the zero page stored in RAM.

This address decoding is superior to the one presented with the 738 decoder because it's actually using the rw and phase 2 lines to correctly assign the read and write cycles for both the ROM and RAM. Doing the address decoding this way should make the system more stable as well as provide a better framework for future IO expansion. This is explained a little better here:

<http://forum.6502.org/viewtopic.php?f=12&t=3214>

<http://forum.6502.org/viewtopic.php?t=168>

<http://forum.6502.org/viewtopic.php?t=511>

For another address decoding example you can check out:

<http://www.6502.org/users/garth/projects.php?project=1&schematic=2>

http://wilsonminesco.com/6502primer/addr_decoding.html

In future revisions I may consider swapping out the 74ls00 with something that can accommodate higher speeds, like maybe something from the 74hc or even better 74ac family(<http://www.digikey.com/product-search/en?mpart=CD74AC00E&vendor=296>).

With this setup our reset vector is at 7FFC/7FFD and contains address C000. Since our ROM only sees the lower 15 lines, this address gets translated to 4000 on the ROM, so that's where we place our code. You can use the same program as above to test the ROM again, only replace the jump to 8000 with C000. ie

```
00004000 a9 12 4c 00 c0 00 00 00 00 00 00 00 00 00 00 00
```

I made this little program to test the RAM:


```
LDX #$FF
STX $3000 ;$3000 = #$FF
```


```
main: LDX $3000
DEX
STX $3000
JMP main
```

essentially this stores FF at RAM location 3000 and then decrements it and stores the value in back in the x register. After assembling this code I made sure the address for main after jmp was pointing to C005 which is the address where the instruction LDX \$3000 begins.

```
00004000 a2 ff 8e 00 30 ae 00 30 ca 8e 00 30 4c 05 c0 00
```

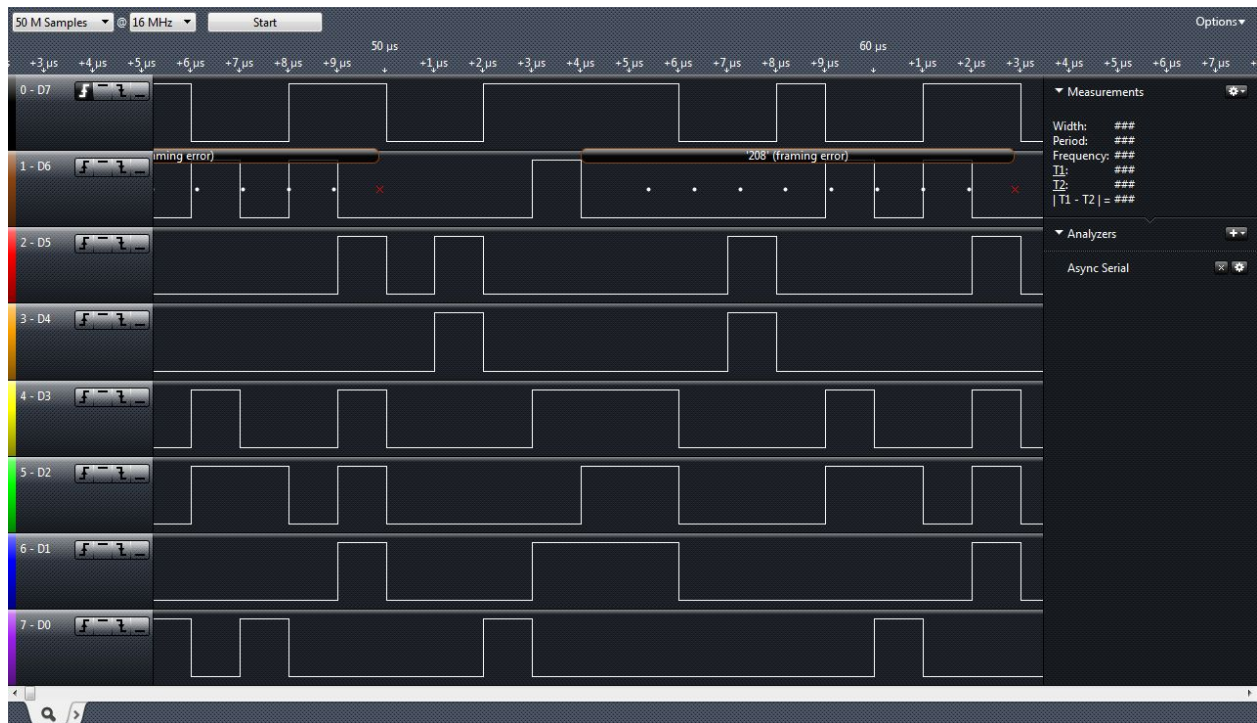then all that was left to do was hook up the logic analyzer to the data bus and see if the decrement was happening, which it was! yay!



 

Connecting an ACIA (MC6850)

A good rundown of how the 6850 is setup is found here: <http://alanclements.org/serialio.html>
datasheet for MC6850: <http://dev-docs.atariforge.org/files/MC6850.pdf>
<https://books.google.com/books?id=YMyjBQAAQBAJ&pg=PA157&lpg=PA157&dq=acia+6850+example&source=bl&ots=LQs-rqLIVx&sig=wY1piDFI7EmCYBK8JsvLpax8dBI&hl=en&sa=X&ved=0ahUKEwjX-Mi50vnJAhUK7mMKHWdACEI4ChDoAQgoMAI#v=onepage&q=acia%206850%20example&f=false> (some example 6502 code to interface with the 6850)

Connecting an ACIA (65c51)

<http://forum.6502.org/viewtopic.php?f=4&t=2543&start=30> (shows workaround for errata wdc version)
connect 65c51 as described here (ignore address decoding logic though):
<http://www.grappendorf.net/projects/6502-home-computer/acia-serial-interface-hello-world>

Here's the finished code which writes Hello World out on the serial line @ 19200 baud.

```
.setcpu "65C02"

ACIA_DATA = $A000
ACIA_STATUS = $A001
ACIA_COMMAND = $A002
ACIA_CONTROL = $A003

;.segment "VECTORS"

;.word nmi
;.word reset
;.word irq

.code

;reset:                jmp main

;nmi:                  rti

;irq:                 rti

main:
init_acia:            lda #00001011                ;No parity, no echo,
no interrupt                                     ;1 stop bit, 8
                                                    data bits, 19200 baud
                                                    sta ACIA_COMMAND
                                                    lda #00011111
                                                    sta ACIA_CONTROL

write:                ldx #0
next_char:
wait_txd_empty:      lda ACIA_STATUS
                    ;and #$10
                    ;beq wait_txd_empty
                    lda text,x
                    beq read
                    sta ACIA_DATA
                    inc
                    jsr DELAY_6551
                    jmp next_char
```

```

read:
wait_rxd_full:      lda ACIA_STATUS
                    and #$08
                    beq wait_rxd_full
                    lda ACIA_DATA
                    jmp write

text:                .byte "Hello World!", $0d, $0a, $00

```

```

DELAY_6551: PHY     ;Save Y Reg
              PHX     ;Save X Reg
DELAY_LOOP: LDY #2   ;Get delay value (clock rate in MHz 2 clock cycles)
;
MINIDLY: LDX #$68   ;Seed X reg
DELAY_1:  DEX       ;Decrement low index
          BNE DELAY_1 ;Loop back until done
;
          DEY       ;Decrease by one
          BNE MINIDLY ;Loop until done
          PLX       ;Restore X Reg
          PLY       ;Restore Y Reg
DELAY_DONE: RTS



```

And here's the compiled binary

004000:	A9	0B	8D	02	A0	A9	1F	8D	03	A0	A2	00	AD	01	A0	BD
004010:	2B	C0	F0	0A	8D	00	A0	E8	20	3A	C0	4C	0C	C0	AD	01	+..... :.L....
004020:	A0	29	08	F0	F9	AD	00	A0	4C	0A	C0	48	65	6C	6C	6F	.).....L..Hello
004030:	20	57	6F	72	6C	64	21	0D	0A	00	5A	DA	A0	02	A2	68	World!...Z....h
004040:	CA	D0	FD	88	D0	F8	FA	7A	60	00	00	00	00	00	00	00z`.....

And the reset vector:

007FD0:	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00
007FE0:	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00
007FF0:	00	00	00	00	00	00	00	00	00	00	00	00	00	00	C0	00	00

 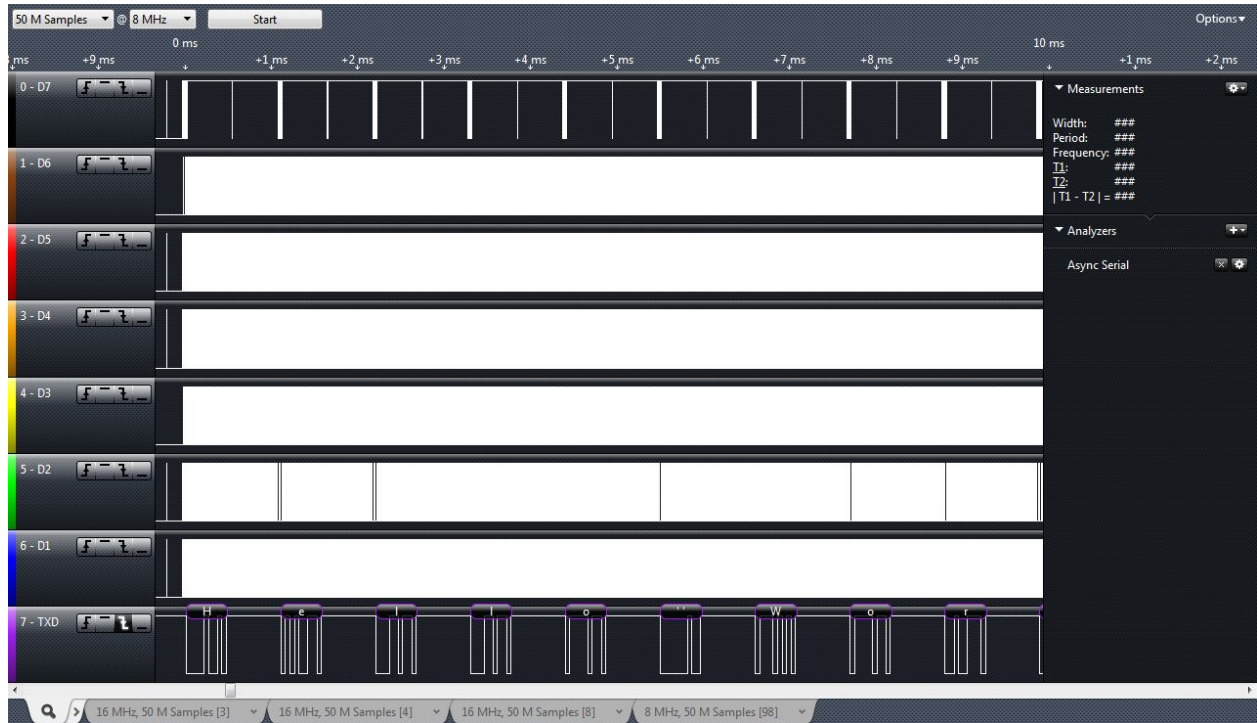

Todo: should I wire acias rtsb to its own ctsb? Also need to probably have parity checking etc.

IO Expansion

might use something like these 3-8 decoders:

<http://www.digikey.com/product-search/en?mpart=74AC11138N&vendor=296> (faster but more expensive.)

<http://www.digikey.com/product-search/en?mpart=CD74AC138E&vendor=296> (slower but cheaper.)

I'm thinking of shifting around the memory map a bit possibly to expand my rom a bit and still provide plenty of IO, see post here: <http://forum.6502.org/viewtopic.php?f=4&t=3211&start=0>

I may try to get a faster eeprom:

<http://www.digikey.com/product-search/en?pv143=17&FV=fff40027%2Cfff80434%2C23c0005%2C23c0011%2Cf040002&mnonly=0&newproducts=0&ColumnSort=0&page=1&stock=1&quantity=0&ptm=0&fid=0&pageSize=25>

<http://www.digikey.com/product-detail/en/AT28HC64B-70JU/AT28HC64B-70JU-ND/1914233>

To prototype this section of the computer I'm sticking with the sn74ls138 3 to 8 demultiplexer, which is a pin compatible although slower version of the CD74AC138E chip. My current memory map includes approximately 8k of free space between \$8000-\$9FFF, which will encompass my IO ports. Using the sn74ls138 allows me to add up to 8 IO devices with just a single chip. To get a better understanding of where the sn74ls138 will go and how it will divide up the memory for our IO devices, let's take a look at our current memory map:

```
RAM START ($0000)      = 0000 0000 0000 0000
RAM END ($7FFF)        = 0111 1111 1111 1111
FREE SPACE START ($8000) = 1000 0000 0000 0000
FREE SPACE END ($9FFF)  = 1001 1111 1111 1111
SERIAL START ($A000)    = 1010 0000 0000 0000
SERIAL END ($BFFF)     = 1011 1111 1111 1111
ROM START ($C000)      = 1100 0000 0000 0000
ROM END ($FFFF)        = 1111 1111 1111 1111
```


To begin thinking about how we're going to provide address decoding to our free space (\$8000-\$9FFF) we need to take a look at how the address lines that make up that space are unique. Typically you want to hook up your address decoding to the last 3 or 4 address lines on the bus, so A15-A12, so let's look specifically at those values. To do this we'll look at the address space

immediately preceding the free space, as well as the one immediately following it.

	A15	A14	A13	A12
RAM END (\$7FFF)	0	1	1	1
FREE START (\$8000)	1	0	0	0
FREE END (\$9FFF)	1	0	0	1
SERIAL START (\$A000)	1	0	1	0

Now, looking at these address lines, what can we see that would differentiate our free space that we want to decode versus the space surrounding it? First off we notice that A15 in our free space always is a 1, whereas our RAM section holds a 0 at A15. This isn't enough to completely differentiate free space from our serial start address though, since serial also has a 1 in A15. Next we can see that A13 for free space is always 0, whereas the other 2 sections are 1. In addition, A14 in free space is always 0. Using this information we can see that in order to decode our free space memory, we need our address decoder to check that A15 is 1, as well as A14 and A13 are 0. So, how do we accomplish this? Checking the datasheet for the SN74LS138, we can see that there are 3 enable pins which can create the glue logic we need.

logic diagram (positive logic)

 

FUNCTION TABLE


ENABLE INPUTS			SELECT INPUTS			OUTPUTS							
G1	$\overline{G2A}$	$\overline{G2B}$	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	X	H	H	H	H	H	H	H	H
X	X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	L	H	H	H	H	H	L	H	H	H	H
H	L	L	H	L	L	H	H	H	H	L	H	H	H
H	L	L	H	L	H	H	H	H	H	H	L	H	H
H	L	L	H	H	L	H	H	H	H	H	H	L	H
H	L	L	H	H	H	H	H	H	H	H	H	H	L

As you can see, G1, G2A, and G2B are used to enable the output of the SN74LS138. We can use these pins to come up with the logic needed to decode our free space. First off the outputs are only enabled when G1 is high (logic 1), so we can tie A15 to G1 since we know that needs to always be a 1 for our free space section. Now we just need to ensure that A14 and A13 are both 0. We can see from the function table above that G2A and G2B need to both be low in order for the outputs to be enabled. This works out perfectly for us if we tie A14 to G2A and A13 to G2B, since both those address lines will be low in our address map. Using this address decoding method, we now have everything we need to decode our free space.

Now that we have our enable pins figured out on our SN74LS138, we need to figure out where to hook up the A,B,C inputs in order to enable the specific Y0-Y7 chip select pin that we need. From the function table above we can see that the A,B, and C pins determine which one of the 8 Y output pins will be set low. By connecting A8 to A, A9 to B, and A10 to C, we can come up with the following IO Decoding table:

		C	B	A
		A10	A9	A8
VIA1	IO1(\$8000)	0	0	0
VIA2	IO2(\$8100)	0	0	1
SID	IO3(\$8200)	0	1	0
	IO4(\$8300)	0	1	1
	IO5(\$8400)	1	0	0
	IO6(\$8500)	1	0	1
	IO7(\$8600)	1	1	0
	IO8(\$8700)	1	1	1

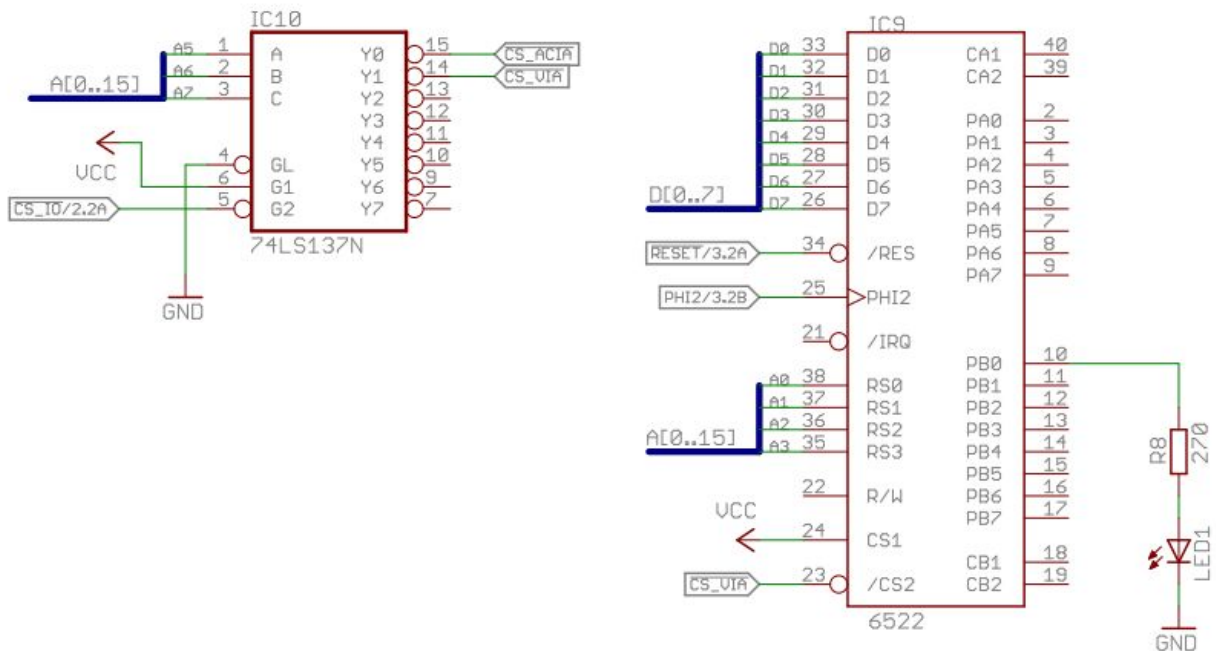With this knowledge we are ready to hook up our vias. For both vias, connect them as shown here:



For CS2, run them to the appropriate Y connector of the SN74LS138 (Y0 to Via1 and Y1 to Via2).

On the final board I want to add jumpers from the irq pin of the 6522 to choose to connect the pin to either the nmi or irq pin of the 6502. Note, that I should be able to chain these irq lines together, as long as I choose the right kind of 65c52 (I think it's 65c52s ...?).

Next I wrote this little program to test the 2 vias. It should cause PB0(pin10) and PB1(pin11) to blink.

```
.setcpu "65C02"

VIA1_DDRB = $8022
VIA1_ORB = $8020
VIA1_DDRA = $8023
VIA1_ORA = $8021
VIA2_DDRB = $8122
VIA2_ORB = $8120
VIA2_DDRA = $8123
VIA2_ORA = $8121

.segment "VECTORS"

.word nmi
.word reset
```

```

        .word  irq

        .code

reset:  jmp  main

nmi:   rti

irq:   rti

main:  lda  #$ff
       sta VIA1_DDRB
       sta VIA2_DDRB

loop:  lda  #$01
       sta VIA1_ORB
       sta VIA2_ORB
       jsr delay
       lda  #$02
       sta VIA1_ORB
       sta VIA2_ORB
       jsr delay
       jmp loop

delay:  ldx  #200
@delay2: ldy  #0
@delay1: dey
        bne @delay1
        dex
        bne @delay2
        rts

```

And here's the config file:

#check out <http://www.cc65.org/doc/ld65-5.html> for info on this config

```

MEMORY
{
  ROM: start=$8000, size=$8000, type=ro, define=yes, fill=yes, file=%O;
}

```


```

SEGMENTS

```


 
```
{  
  CODE: load=ROM, type=ro, offset=$4000;  
  VECTORS: load=ROM, type=ro, offset=$7FFA;  
}
```




Adding an LCD

Now that we have the IO figured out and the 2 VIAs connected, we can move on to adding an lcd!

I chose the HD44780 lcd chipset, since I already had a couple lying around. The one I hooked up was from an old 90s printer I salvaged! These lcds are also fairly common today. I included links to datasheets and other sites that helped me interface with it in the resources section.

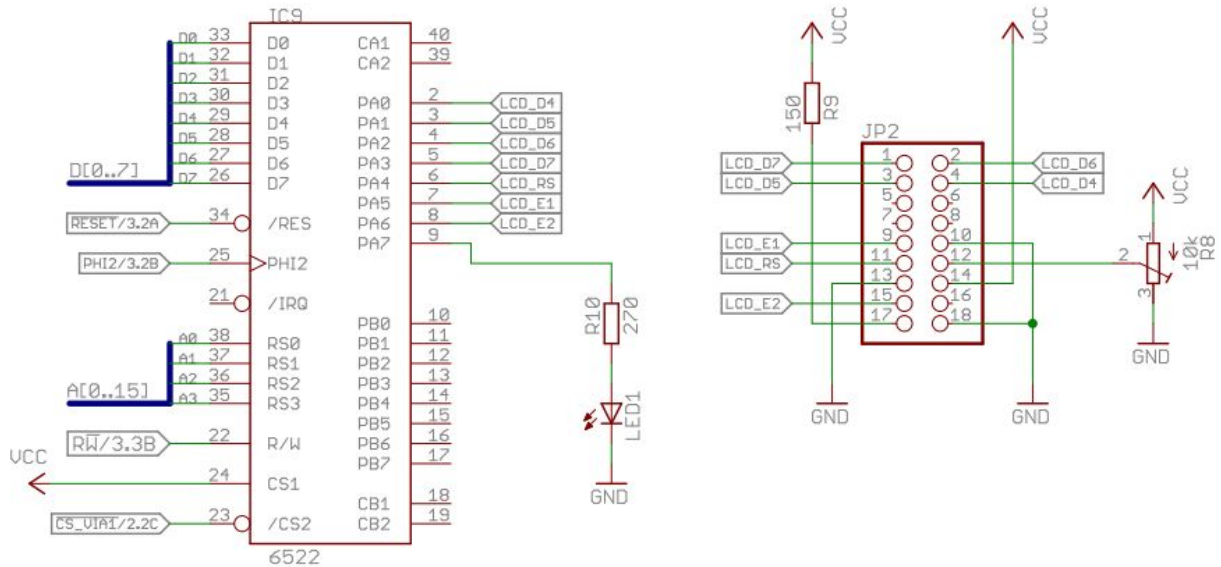To start out with I connected VIA2 to the lcds data, register select, and enable lines as shown here:



Note that in my case I didn't need to connect an E2(Enable 2) pin, since my lcd only has 2 lines, and therefore only had one enable pin. So just ignore the connection going from PA6(pin 8) of the via.

Here's a little program I wrote to show how to initialize the lcd and write out "Hello World" on the screen:

```
.setcpu "65c02"
.include "macros.inc65"

.include "io.inc65"

LCD_D4 = VIA_PA0
LCD_D5 = VIA_PA1
LCD_D6 = VIA_PA2
LCD_D7 = VIA_PA3
LCD_RS = VIA_PA4
LCD_EN1 = VIA_PA5
LCD_EN2 = VIA_PA6
```

```
enable_bits: .byte 0

.segment "VECTORS"
```

```

        .word   nmi
        .word   reset
        .word   irq

        .code

reset:           jmp main

nmi:            rti

irq:           rti

main:

                jmp lcd_init2

loop:

lcd_init2:      jmp loop

                lda   #$ff
                sta   VIA2_ORA
                sta   VIA2_DDRA
                ldx   #50
                jsr   delay_ms

                ;set register select bit to 0 for command/control

                ;start init sequence
                lda   #$03
                jsr   strobe_enable
                ldx   #5
                jsr   delay_ms

                lda   #$03
                jsr   strobe_enable
                ldx   #5
                jsr   delay_ms

                lda   #$03
                jsr   strobe_enable
                ldx   #5
                jsr   delay_ms

                lda   #$02
                jsr   strobe_enable

```

```
ldx #3
jsr delay_ms

;now in 4 bit mode

;function set
lda #$02 ;set data length to 4 bits
jsr strobe_enable

;no delay needed here

lda #$08 ;2 lines 5x8 pixels
jsr strobe_enable
ldx #3
jsr delay_ms

lda #$00 ;turn display off
jsr strobe_enable
lda #$08
jsr strobe_enable
ldx #3
jsr delay_ms

lda #$00 ;clear display
jsr strobe_enable
lda #$01
jsr strobe_enable
ldx #3
jsr delay_ms

lda #$00 ;entry mode set
jsr strobe_enable
lda #$06
jsr strobe_enable
ldx #3
jsr delay_ms
;end of initialization

lda #$00 ;turn display on
jsr strobe_enable
lda #$0f ;display on, cursor on, blink on
jsr strobe_enable
ldx #3
jsr delay_ms

lda #$00 ;CURSOR HOME
```



```
jsr strobe_enable
lda #$02 ;cursor home
jsr strobe_enable
ldx #3
jsr delay_ms

jmp write_hello_world
```

write_hello_world:

```
    ;send H
lda #$14
jsr strobe_enable
ldx #5
jsr delay_ms

lda #$18
jsr strobe_enable
ldx #5
jsr delay_ms

;send E
lda #$14
jsr strobe_enable
ldx #5
jsr delay_ms

lda #$15
jsr strobe_enable
ldx #5
jsr delay_ms

;add in extra strobe for reading 8 status bits
lda #00
jsr strobe_enable
lda #00
jsr strobe_enable

;send L
lda #$14
jsr strobe_enable
ldx #5
jsr delay_ms

lda #$1C
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
;send L
lda #$14
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
lda #$1C
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
;send 0
lda #$14
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
lda #$1F
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
;send space
lda #$12
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
lda #$10
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
;send W
lda #$15
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
lda #$17
jsr strobe_enable
ldx #5
jsr delay_ms
```

```
;send 0
lda #$14
jsr strobe_enable
ldx #5
```

```
jsr delay_ms

lda #$1F
jsr strobe_enable
ldx #5
jsr delay_ms

;send R
lda #$15
jsr strobe_enable
ldx #5
jsr delay_ms

lda #$12
jsr strobe_enable
ldx #5
jsr delay_ms

;send L
lda #$14
jsr strobe_enable
ldx #5
jsr delay_ms

lda #$1C
jsr strobe_enable
ldx #5
jsr delay_ms

;send D
lda #$14
jsr strobe_enable
ldx #5
jsr delay_ms

lda #$14
jsr strobe_enable
ldx #5
jsr delay_ms

;send !
lda #$12
jsr strobe_enable
ldx #5
jsr delay_ms

lda #$11
jsr strobe_enable
```

```

        ldx #5
        jsr delay_ms

        jmp loop

strobe_enable:
        ora #$20      ;add enable bit
        sta VIA2_ORA ;send value out to via
        ldx #10
        jsr delay_ms
        and #$DF     ;mask to take out enable
        sta VIA2_ORA ;take out enable bit and send to via

        rts

; Delay the number of miliseconds specified by X
; This is hardcoded for a 1 MHz system clock
delay_ms: pha      ; 3
          txa      ; 2
          pha      ; 3
          tya      ; 2
          pha      ; 3

          ldy $00  ; 3 (dummy operation)
          ldy #190 ; 2
@loop1:  dey      ; 190 * 2
          bne @loop1 ; 190 * 3 - 1


@loop2:  dex      ; 2
          beq @return ; (x - 1) * 2 + 3

          nop      ; 2
          ldy #198 ; 2
@loop3:  dey      ; 198 * 2
          bne @loop3 ; 198 * 3 - 1

          jmp @loop2 ; 3

@return: pla      ; 4
          tay      ; 2
          pla      ; 4
          tax      ; 2
          pla      ; 4
          rts      ; 6 (+ 6 for JSR)

```

 

resources:

<https://www.sparkfun.com/datasheets/LCD/HD44780.pdf>


http://web.stanford.edu/class/ee281/handouts/lcd_tutorial.pdf

<https://www.arduino.cc/en/Tutorial/HelloWorld>

<http://www.bipom.com/documents/appnotes/LCD%20Interfacing%20using%20HD44780%20Hitachi%20chipset%20compatible%20LCD.pdf>

http://web.alfredstate.edu/weimandn/lcd/lcd_initialization/lcd_initialization_index.html

Adding SID (sound interface device) Chip

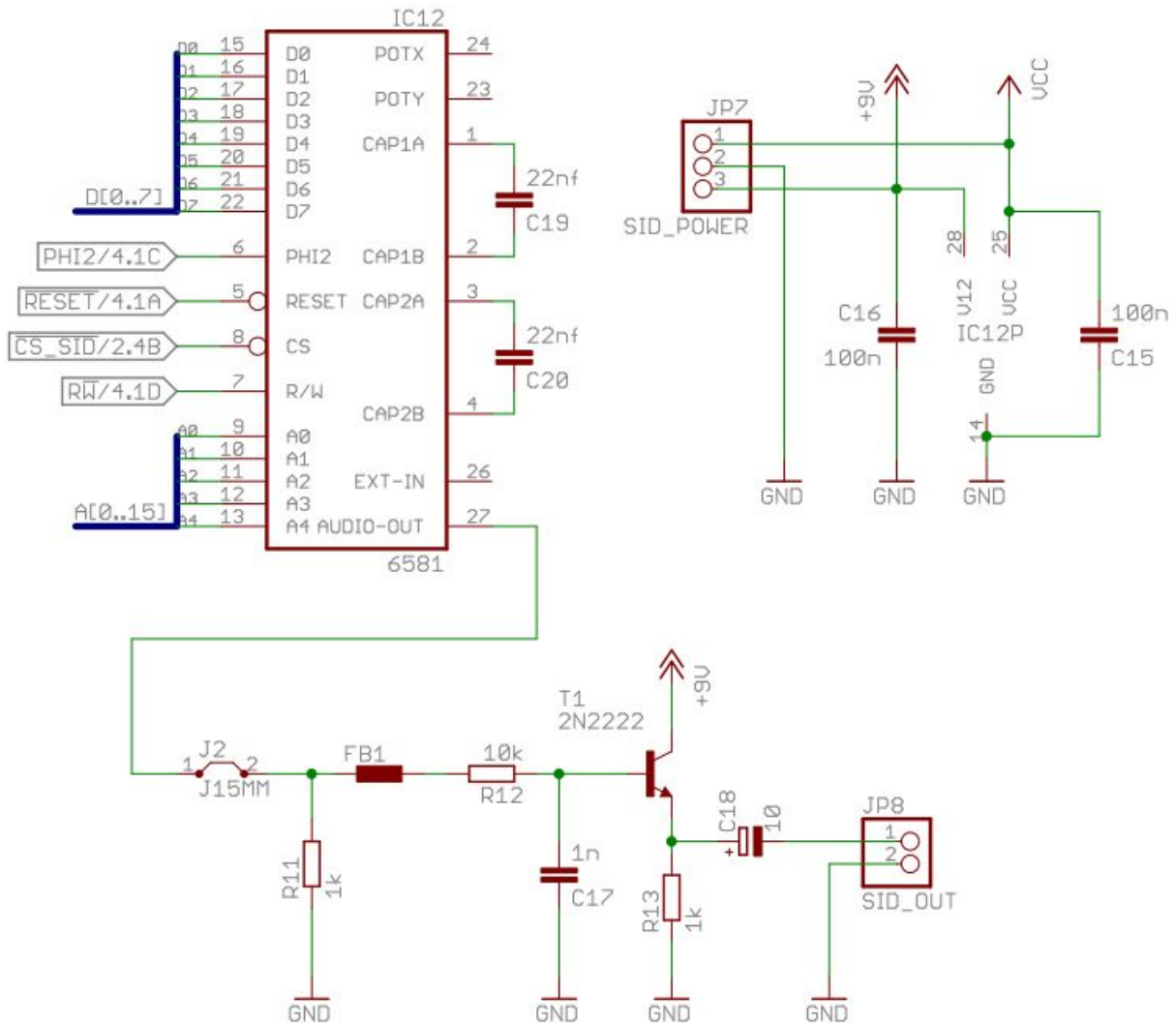

For the audio out circuitry I stuck a 1k resistor from the 6581 pin 27 to ground and then ran the signal over to an amplifier built from an Im386 circuit found here: <https://www.youtube.com/watch?v=PPQ87kjEgBA> . I was thinking on the eventual board I could stick a switch between the gain boost 10uf cap and the resistor between pins 1 and 8 of the Im386. This would allow me to turn the gain on for driving large speakers, but then turn it off when listening to headphones etc. Instead of an Im386, since those are now obsolete, I could use this chip: <http://www.digikey.com/product-detail/en/NJM386D/NJM386D-ND/805736>, which is a drop in replacement for the Im386.

resources:

<http://www.grappendorf.net/projects/6502-home-computer/sid-sound.html>

<http://www.acsu.buffalo.edu/~robertsz/projects/SID/index.html>

http://archive.6502.org/datasheets/mos_6581_sid.pdf

http://www.deblauweschicht.nl/tinkering/mos6581_1.html

<http://www.sidmusic.org/sid/sidtech3.html> (For best results, the ground line between SID and the power supply should be separate from ground lines to other digital circuitry. This will minimize digital noise at the audio output.)

On another forum I read that you should ground the ext-in pin of the sid if it was not being used. This should prevent extra noise from entering the system.

<http://csdb.dk/forums/index.php?roomid=7&topicid=36766&showallposts=1>

This method is pretty effective atleast on 6581 chips, it insulates 6581 from the data and address busses when CS (Chip select) line for sid is not active.

Combined with filtered and separate +12v and +5v voltages and own separate grounding it improves output quality alot. Also grounding potx, poty and ext-in lines with small (1nF) capacitor helps littlebit on the way. Also building separate audio out buffer (pre amp) and making own audio out connector helps on the way too.

<http://www.lemon64.com/forum/viewtopic.php?t=47932&sid=5920081b88b25de7e4688e5584dcfafe>

<http://www.commodore64site.nl/schematics/251469-1of2.gif>

https://www.c64-wiki.com/images/5/5b/PRG_Schematic_%28right%29.gif

(c64 schematic showing sid circuitry)

also 8580 sid chip (later version of 6581)

another possible sound chip: https://en.wikipedia.org/wiki/General_Instrument_AY-3-8910

AY-3-8910, AY-3-8912, YM2149

YM2203

Adding Compact Flash

resources:

<https://www.sparkfun.com/datasheets/BreakoutBoards/c0201mspdf.pdf>

<http://read.pudn.com/downloads52/ebook/178846/S72032.pdf>

<http://forum.6502.org/viewtopic.php?f=4&t=2877>

<http://www.msarnoff.org/6809/>

<https://www.sparkfun.com/datasheets/BreakoutBoards/c0201mspdf.pdf>

http://rumkin.com/reference/aquapad/media/cfspc3_0.pdf

<http://sbc.rictor.org/io/IDE.html>

<http://dreher.net/?s=projects/CFforApple1&c=projects/CFforApple1/main.php>

<https://cowgod.org/replica1/applesoft/>

<http://www.microchip.com/forums/m364311.aspx>

http://elm-chan.org/fsw/ff/00index_e.html

Adding a Keyboard

Should I use a decade counter?

https://mechanicalkeyboards.com/shop/index.php?l=product_list&c=40&show=100

Adding a Case

polycase.com

<https://www.shapeways.com/model/upload-and-buy/4251306#materials>

<http://www.makexyz.com/help/faq>

<https://www.3dhubs.com/3dprint#?place=639%20Weaver%20Hill%20Ln,%20Colfax,%20CA%20095713,%20USA&latitude=39.012399599999995&longitude=-120.976127299999997&distanceUnit=miles>

<http://www.ponoko.com/home>

<http://lasergist.com/>

protocase.com


emachineshop.com

bigbluesaw.com

<https://learn.adafruit.com/laser-cut-enclosure-design/overview>

<http://parts-badger.com/>

 something like this: <https://www.adafruit.com/products/859>



I'm thinking of naming it STACHE I. And making the lettering in 8 bit with a 3d texture (like http://orig05.deviantart.net/ae1f/f/2013/265/1/8/8_bit_moustaches__the_wario_by_mattcantdraw-d6ncbh5.jpg).

Or another name might be RETRO I. or retro 1 (all lowercase like apple ii)

Adding BASIC

<http://www.asciimation.co.nz/bb/2013/10/02/orwell-keyboard-input-and-basic>

Adding real time clock

<https://github.com/ytmytm/c64-ds12c887>

<https://courses.engr.illinois.edu/ece391/references/mc146818.pdf>