

STUPID

Steve Toner
(solo)
Fall 1978

Course 6-112 term project

Abstract

STUPID (Simple Twelve-bit Unadorned Programmed Instruction Decoder) is a twelve bit microprogrammed single address, single accumulator computer which does not resemble the PDP-8.

Introduction & Overview

The STUPID instruction set closely resembles that of the "Little Man Computer" of 15.564. Instructions have a 4-bit op code and 8-bit address. STUPID is a binary machine, while the Little Man Computer is a decimal machine. The STUPID instruction set is (all numbers in hexadecimal):

000 - HALT

1XX - ADD: Add the contents of memory location XX to the AC

2XX - SUB: Subtract the contents of location XX from the AC

3XX - AND: Logical bit-wise and (XX) with AC

4xx - OR: Logical bit-wise or (XX) with AC

5XX - CLEAR: Clear memory location XX

6XX - ISZ: Increment XX and skip the next instruction if
the result = 0

7XX - DSZ: Decrement XX and skip if result=0

8XX - LOAD: Load the AC with the contents of XX

9XX - STORE - Deposit the AC in location XX

AXX - HANG: Hang the processor

BXX - BRANCH: Branch to location XX

CXX - BZ: Branch if (AC)=0

DXX - BN: Branch if (AC)<0

EXX - BP: Branch if (AC)>0

F0X - NOP*

F1X - GCHAR: Read a character from the TTY

F2X - PCHAR: Type the character in AC on the TTY

F3X - RSWR: Read contents of switch register into AC

F4X-FFX - NOP*

*These are "reserved for future expansion"

The address space of STUPID is only 8 bits and there is no indirect addressing.

There are 5 registers in the STUPID machine: AC, PC, MAR, MBR, MWR. There is also a switch register (SWR) and Teletype out (TTY) "register". AC is the accumulator, where all arithmetic and logical operations leave their result and through which all I/O is performed. PC is the program counter, which functions in the obvious way. MAR is the memory address register, which holds the memory address for all reads from and writes to memory. MBR is the memory buffer register, which receives the data which is read out of memory (and so is a "read only" register). MWR is the memory write register, which holds the data which is to be written into the location specified by the MAR. It is a "write only" register. A block diagram of the system is shown in figure 18. The MBR appears on both the A and B busses, as when we do an "ADD" we will read the value to be added to the AC into the MBR, and then add this to the AC. Therefore the MBR must be on the B bus. But it must also be on the A bus, because we need to be able to add or subtract one from it when doing an ISZ or DSZ. The 74181 ALU gives A plus 1 and A minus 1 directly, but not B plus 1 or B minus 1.

The STUPID control box is microprogrammed. The microcode instruction format is shown in figure 15. There are three types of operations: ALU operations, which move data between registers; branch operations, which control the microprogram

sequencing; and "OP"s, which include everything not covered by the ALU and branch operations. These (OP) operations include reading from memory, writing to memory, dispatching on op code and lighting the "magic mode" light.

The STUPID microcode

The microcode for STUPID is included in Appendix A. Operation is fairly straightforward. When the RESET button is pressed, the microprogram sequencer is cleared and the micro instruction register is set to zero. This assures that the microcode starts at location 0 (a micro instruction of 0 = br 0). At this point the magic mode switch is checked. If it is set, STUPID runs some simple diagnostics. If one of these diagnostics fails, the machine will hang and an address will be displayed in the micro pc lights. Appendix B lists all possible hangs and possible causes for each. If the diagnostics run through without error, STUPID examines the location specified by the SWR and displays it in the AC lights. If the data in this location is to be changed, the new value can be set into the SWR at this point and START pressed. STUPID will deposit the SWR data into the location and increment the PC (In magic mode the PC always shows the current location - that location which will be modified if START is pressed). The new location is displayed and can be modified as before. At this point, if the magic mode switch is turned off, or if it is not on when RESET is pressed, STUPID waits for START to be pressed. When START is pressed, the SWR is loaded into the PC and instruction execution begins. The instruction is fetched, and STUPID dispatches on the op code to the routine which does the particular instruction. That's all there is to the microcode. The only instructions which are not entirely straightforward are ISZ, DSZ and the instructions with

op code F. ISZ and DSZ must test to see if the result of the increment or decrement is zero. Since the MWR is a write only register, it cannot be tested for zero without a lot of special logic. Therefore, ISZ and DSZ do a simultaneous write and read when writing the result back. This puts the result in the MBR which can be tested. But the =0 signal comes from a flip flop which is set only on ALU operations (see figure 2), so isn't it still valid after a write? Yes, but sometimes we don't see the obvious until it's too late. The =0 condition started out as a general A=B condition, but only result=0 was ever used, so it became =0 (the original idea was to use the A=B output of the ALU, but as it turns out that signal is only valid if the right operation is specified, so that got the "deep six" as they say.) In the op F instructions, the second nibble indicates the particular instruction. It is necessary to dispatch on this value, so it must be put into the high order 4 bits of the MBR (where DISP gets its argument). This is accomplished by putting it in the AC and shifting left 4 bits. The original value of the AC is saved in location 00 and read back if the instruction does not put a new value in it (GCHAR, RSWR). Since the instruction bits must be in the MBR to do a dispatch, the shifted value is written into location FF and read back (simultaneously, to save time). Thus, locations 00 and FF should not be used by a program. This awfulness could be alleviated somewhat by adding some temporary registers to the machine, but space limitations dictate that this not be done.

The A and B busses are implemented as multiplexors - A a 4 input mux and B a 2 input mux (see figs 11 & 12). Bits 1 and 2 of an ALU instruction specify which A input to select. Similarly, bits 3 and 4 specify the B input. Two bits here allow for easy expansion, and in fact B_3 is already defined to be the TTY in register. Space constraints limit B to be a 2-input multiplexor, however. Each ALU operation also specifies the carry and function in bits 5-10. These are fed directly to the appropriate inputs on the ALU card (see figure 2 for ALU). This means that a carry in of 1 is specified by a 0 in bit 5, since the MSI 181 has inverted carry signals. The destination register is specified by bits 11-15. Each output register has a bit associated with it, though three bits could be used and these three bits decoded to one of 8. But a decoder is another card and ROM bits are free, provided we don't use more than 16 of them. If the machine were to be expanded to include an index register or other registers, the decoding scheme would have to be used. The destination bit is NANDed with $(\text{BIT}0 \cdot \overline{\phi_2})$ to give the clock input to the MSI 161, which is used for all these registers (except TTY). (see figs 3, 4 & 10) BIT0 tells it that this is an ALU operation, so that bit which looks like a destination bit really is. The two phase clock (see figure 5) is used because the 74161 counter uses master-slave flip flops, and the load input cannot change when the clock line to these is low. Therefore, the micro sequence counter is incremented/loaded on the leading edge of ϕ_2 (see figure 14 for ϕ_1, ϕ_2 timing) and the ROM outputs (which are what cause the load line to change) are

clocked into a register on the leading edge of ϕ_1 . This assures that the sequencer's load line changes only when its clock line is high. Since the data at the ALU outputs is valid sometime after ϕ_1 until the next rising edge of ϕ_1 , $\overline{\phi_2}$ is as good as anything to clock the registers. I am not convinced that the 2-phase clock is necessary, but since the LSI 1702 outputs can drive only 1 load, there has to be something buffering them. The two-phase clock is safe (like it works, so don't knock it). The question is whether the output of the 1702 glitches (can BIT0 go 0→1→0, for example?) when a new address is selected. I don't know, so I assume the worst.

Branches are implemented by putting the inverted value of the condition on the load line of the micro sequencer and the branch address on the data inputs. On the next rising edge of ϕ_2 , the counter will be loaded with the address if the condition was true. Simple. The condition bits (BIT2-4) address a multiplexor and if BIT0=BIT1=0, the condition (inverted) is let through (see figure 1). Otherwise (no branch), the load line is held high so the counter will be incremented.

OPs are decoded by detecting BIT0=0, BIT1=1 (actually BIT0=0 and not BR). This signal is ANDed with the appropriate bit to decode the instructions. This causes a timing problem on a WRITE (you should now be looking at figure 6). Since OP must go through 2 NOR gates, it is delayed from the write signal, which comes directly from BIT15. Thus, if a READ is followed by an instruction which happens to have BIT15 set, BIT15 comes on, OP

is delayed by a couple of gate delays and w goes low, which makes the memory think it supposed to do a write. To fix this problem, gate delays are put on BIT15 (the *'d guys in figure 6) so that it cannot change until after OP has changed. Crude but effective.

A dispatch also causes a branch, so causes the load input of the sequencer to go low. However, this time the address comes only partly from the instruction. The low order 4 bits are specified by the high order 4 bits of the MBR. Only the high order 4 bits of the address are specified by the dispatch instruction.

The Memory

The basic memory box is the same one used in the memory dumper/loader (saves plugging wires if I just use what's already there - there's no point in reinventing the wheel when you've got something that works...). It is shown in figure 9. Each memory operation (read or write 4 bits) takes 7 clock cycles (memory timing shown in figure 13). If the mwrite line is high, the $\overline{T/w}$ line will go high during states writel-write4. Otherwise (on a read) $\overline{T/w}$ is held low. The memory is controlled by a shift register in which a single 1 is shifted right 1 bit on each clock pulse. 574 flip flops were used to construct this shift register, as they can be cleared or set asynchronously, so resetting the register to the idle state can be accomplished painlessly. The register is set to 100000 (leftmost bit corresponds to leftmost FF in figure 9) whenever the RESET button is pressed (as

will hopefully be done on power-up, when the states of the flip flops are unknown). Since the 574 outputs change from L->H faster than H->L, the \bar{r}/w line cannot glitch, which might otherwise cause problems when writing. To read a word (4 bits) from the memory, an address is put on the addr lines and mread is brought high. When resetr/w transitions from H->L, the data on the read data lines is valid. resetr/w is normally used to clock the read data into a register. A write is done by setting up the address and the data to be written and raising mwrite. mread and mwrite must stay high at least until the shift register leaves the idle state. The rising edge of resetr/w may be used to clear mread and mwrite.

STUPID words are 12 bits long, which means that we must read or write 3 4-bit words for each STUPID word (this is necessary because of the restriction of 1 LSI 2102 per person). The memory controller shown in figure 6 accomplishes this monumental task. When a read instruction is executed, \bar{r} goes low. This clears the A and B flip flops and sets the mread FF. The r signal is NANDed with $\overline{\text{memdone}}$ to assure that the clock signal changes after $\overline{\text{memdone}}$ goes high - otherwise the clock transition would be lost. Setting mread causes the memory to read a single 4-bit word as described above. resetr/w is used to clock the A and B flip flops, which count in the sequence 00, 10, 11, 01 (AB). On the 00->10, 10->11 and 11->01 transitions, the read data is latched into the MBR (see figure 7). This means that the read data must stay valid until it can be latched. The LSI 1702 data is valid

for about 100 nsec after the address change, which is plenty of time. In state 01, memdone is asserted and this clears mread. Q_A and Q_B are used as the low order 2 bits of the memory address. A write is similar to a read in the way it clears the A and B FFs and sets mwrite. This time, however, Q_A and Q_B are used to select which nibble of the MWR to apply to the write data lines (see figure 8).

ALU

The ALU is a standard 74181 and the microcode specifies the carry in, M and S_0-S_3 , so any of the ALU functions may be used. Table 1 in figure 16 shows the possible ALU functions.

Rack Layout

The rack layout is shown in figure 99. It didn't fit in a single rack. Figure 99a shows the various lights and switches used...

Summary and conclusions

Well, it works. A demonstration program (which uses all the STUPID instructions except the NOPs, GCHAR and HANG) is included in Appendix C. Read the comments for documentation. At this point, many possible improvements and modifications cry out to be considered. STUPID has a teletype for output, but only a switch register for input. How about adding a TTY in? Originally it appeared that this would require extending the B bus by using 4 input multiplexors instead of 2. However, looking at it now (that it's too late), I see that the zero input on the B bus is not used. The ALU has functions A, A plus 1, etc, which do not require B to be zero, and the A=B instruction was changed to =0. So the TTY in register could replace the zero "register" on the B bus. Once this was done, the microcode could be changed to allow memory to be loaded from a paper tape in the TTY reader. that would make life much easier for the poor soul who has to load a program into memory. Since A=B was changed to =0, the microcode could also be changed so that it doesn't do unnecessary comparisons with zero. Or, since no register has to be specified to receive the result of an operation, the zero comparison could be done by complementing the register which is being tested, specifying no destination, and using the A=B outputs of the ALU instead of the NOR gates that are there now. One way saves time, the other hardware. Other possible changes include changing the instruction set to allow indirect addressing (no change in the hardware is necessary to allow single level indirection - just

some instructions would have to be thrown out) and, if somebody were to decide that he actually wanted to use this (STUPID) machine for something, he might want more memory and more than one I/O device. There are 4 bits which are unused in the GCHAR and PCHAR instructions - these could be turned into more general DATA IN and DATA OUT instructions with the low order 4 bits specifying the device. More condition branching might have to be added to the micro machine to allow this. Finally, what about the HANG instruction and all those NOPS? Some intelligent person ought to be able to come up with something to do with them. Right now they're not very useful.

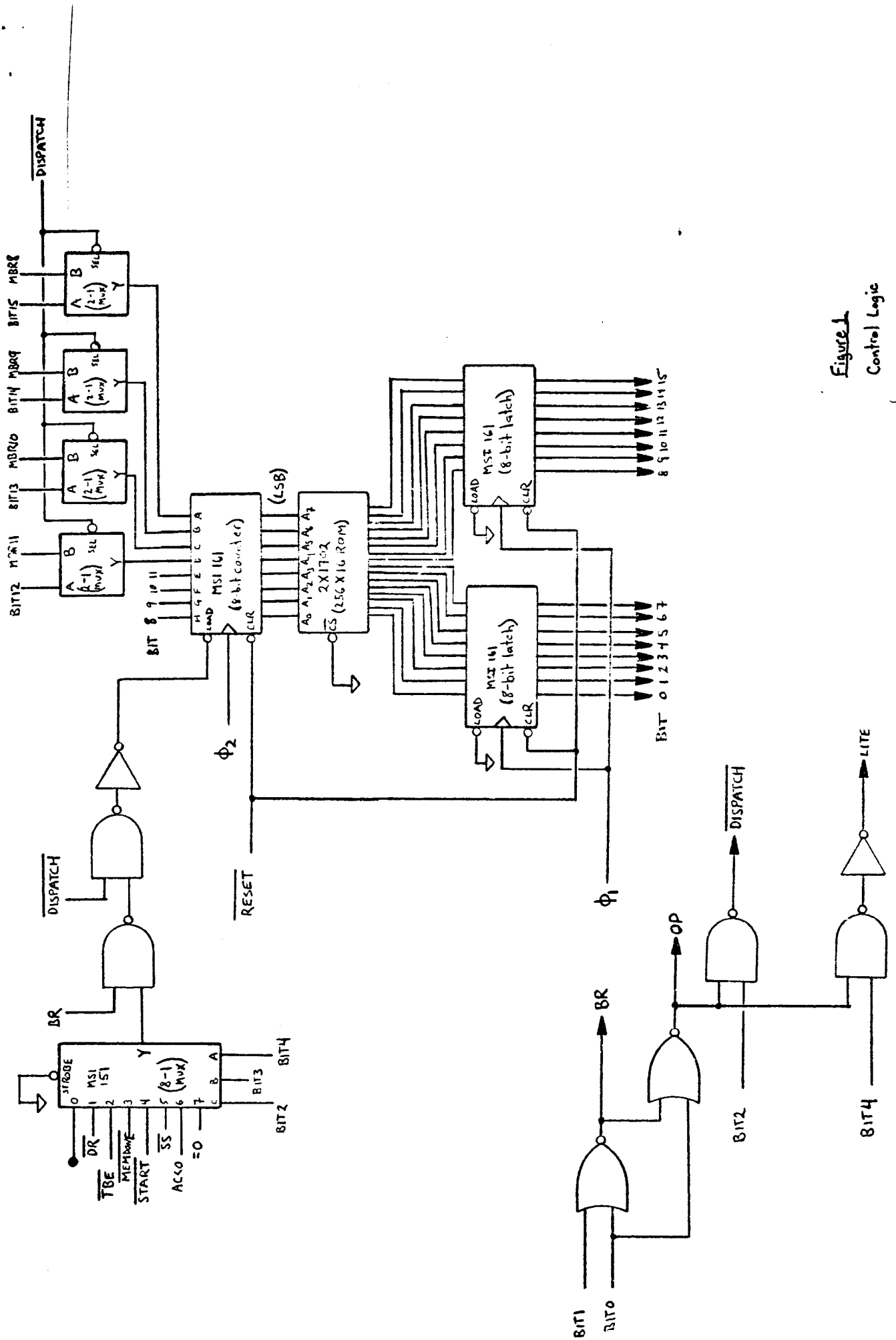


Figure 1
Control Logic

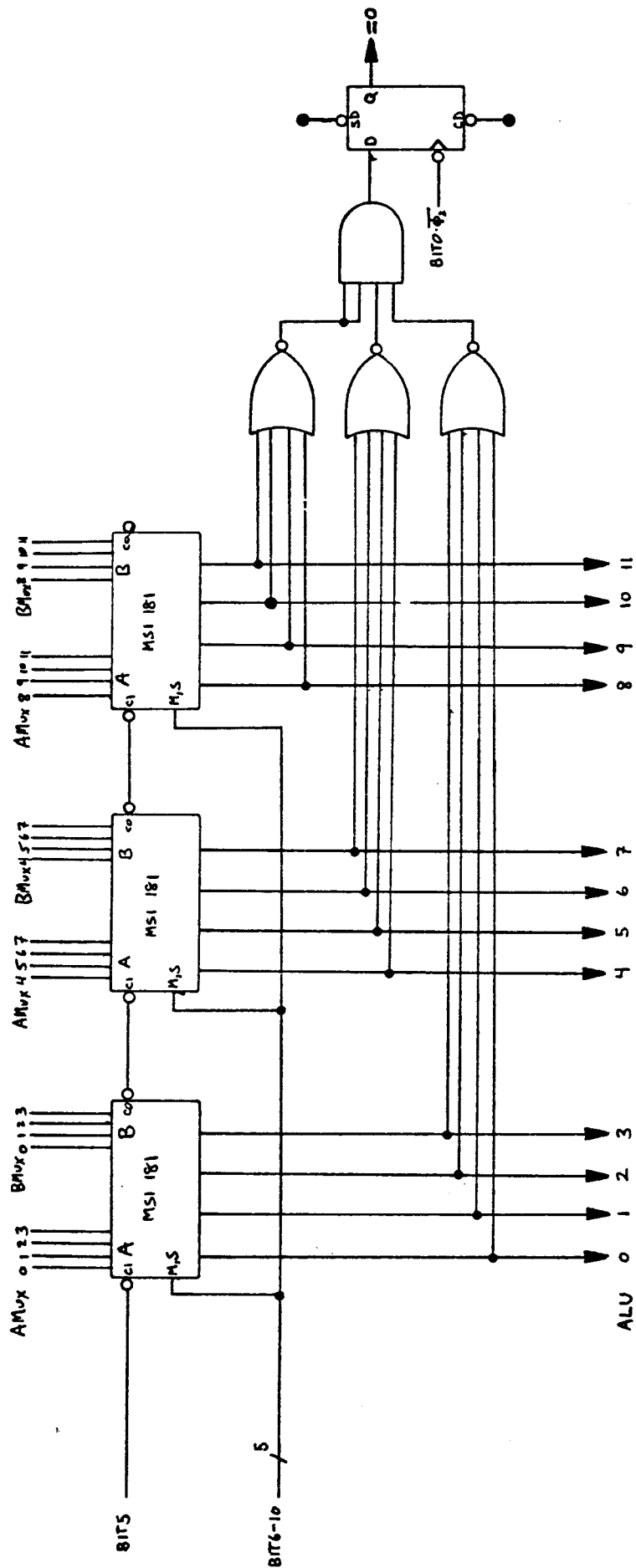


Figure 2
ALU

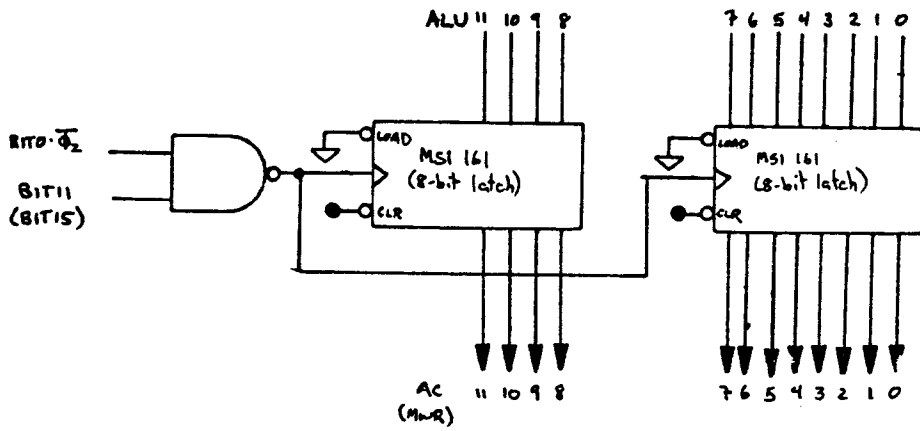


Figure 3
Accumulator, MWR

 


Figure 4
Program Counter, MAR


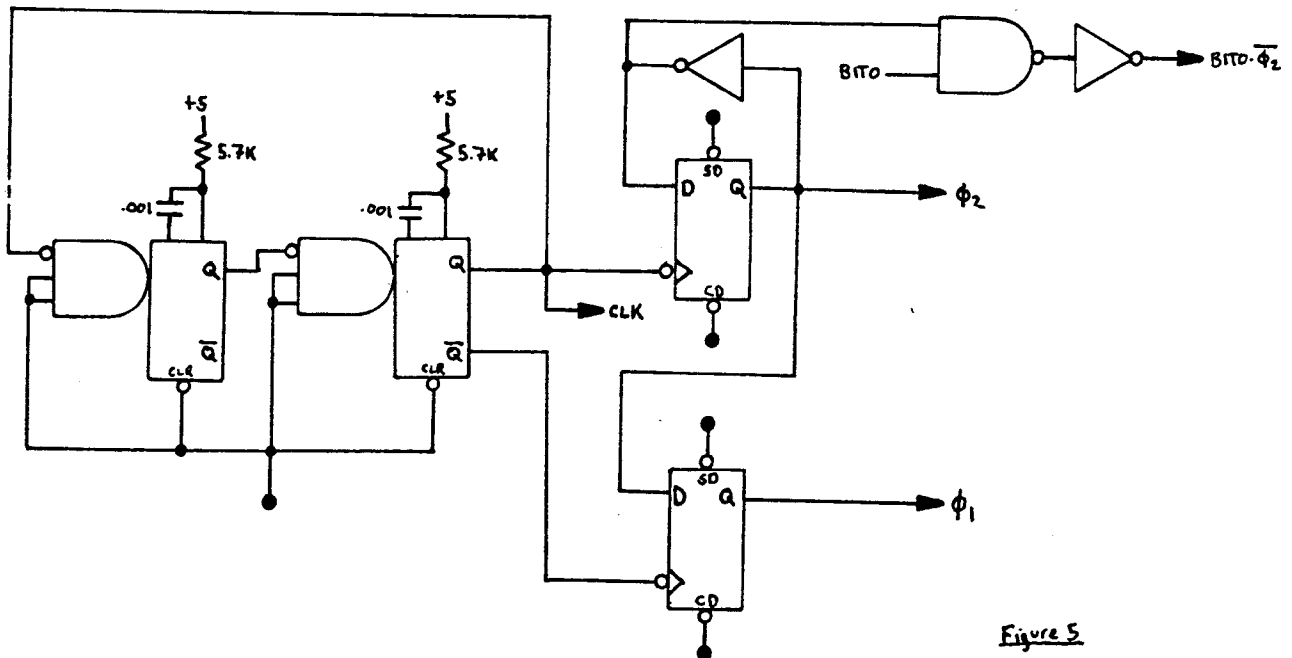
 


Figure 5
Clock

 

COUNT SEQUENCE

A	B
0	0
1	0
1	1
0	1

 


Figure 6
Memory Control

 


Figure 7
Memory Buffer Register

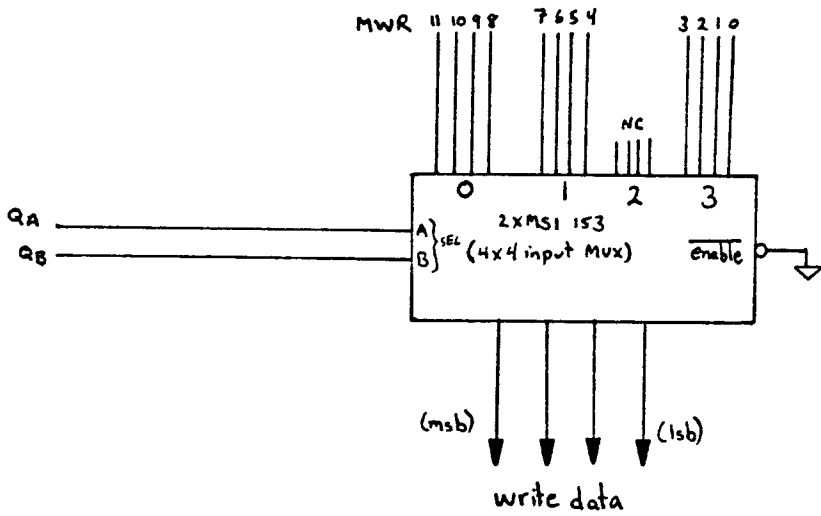


Figure 8

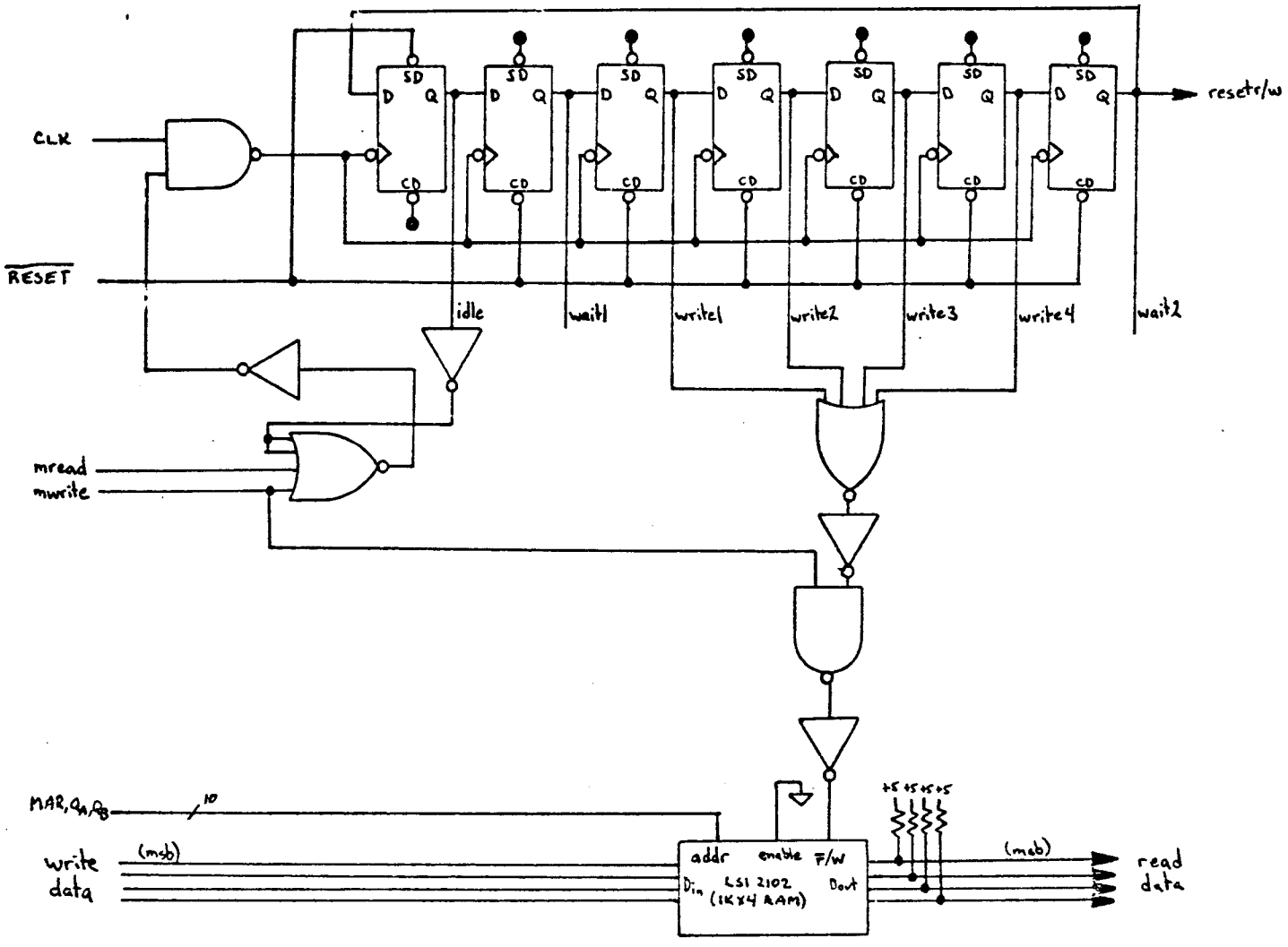


Figure 9
Memory

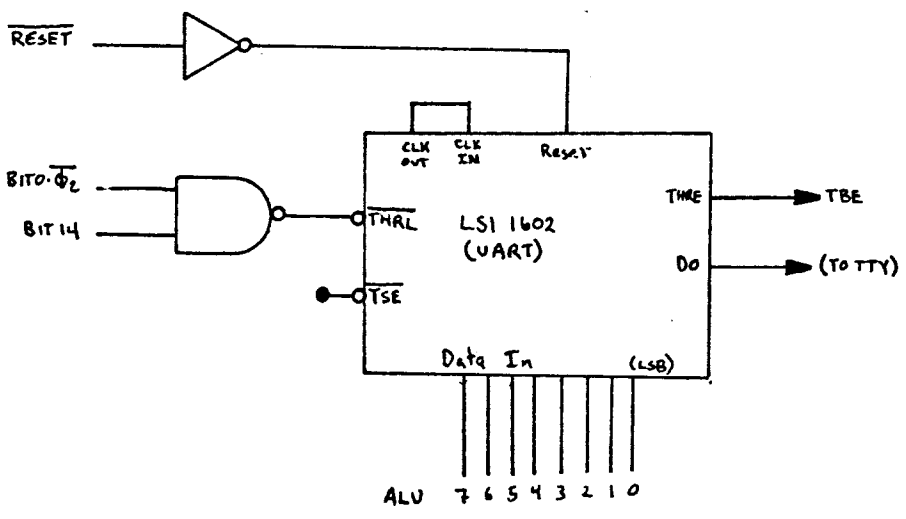


Figure 10
TTY

 


Figure 11
 A Multiplexer


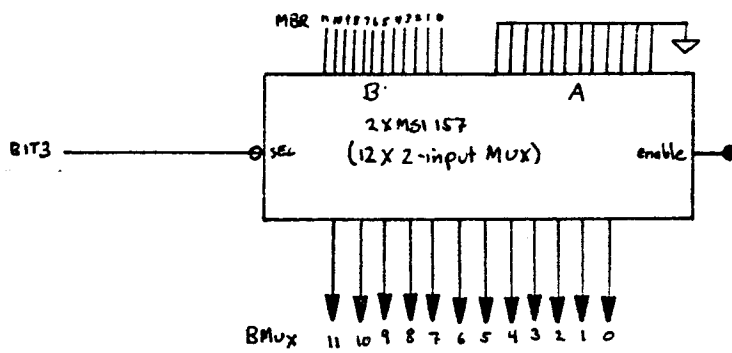


Figure 12
 B Multiplexer

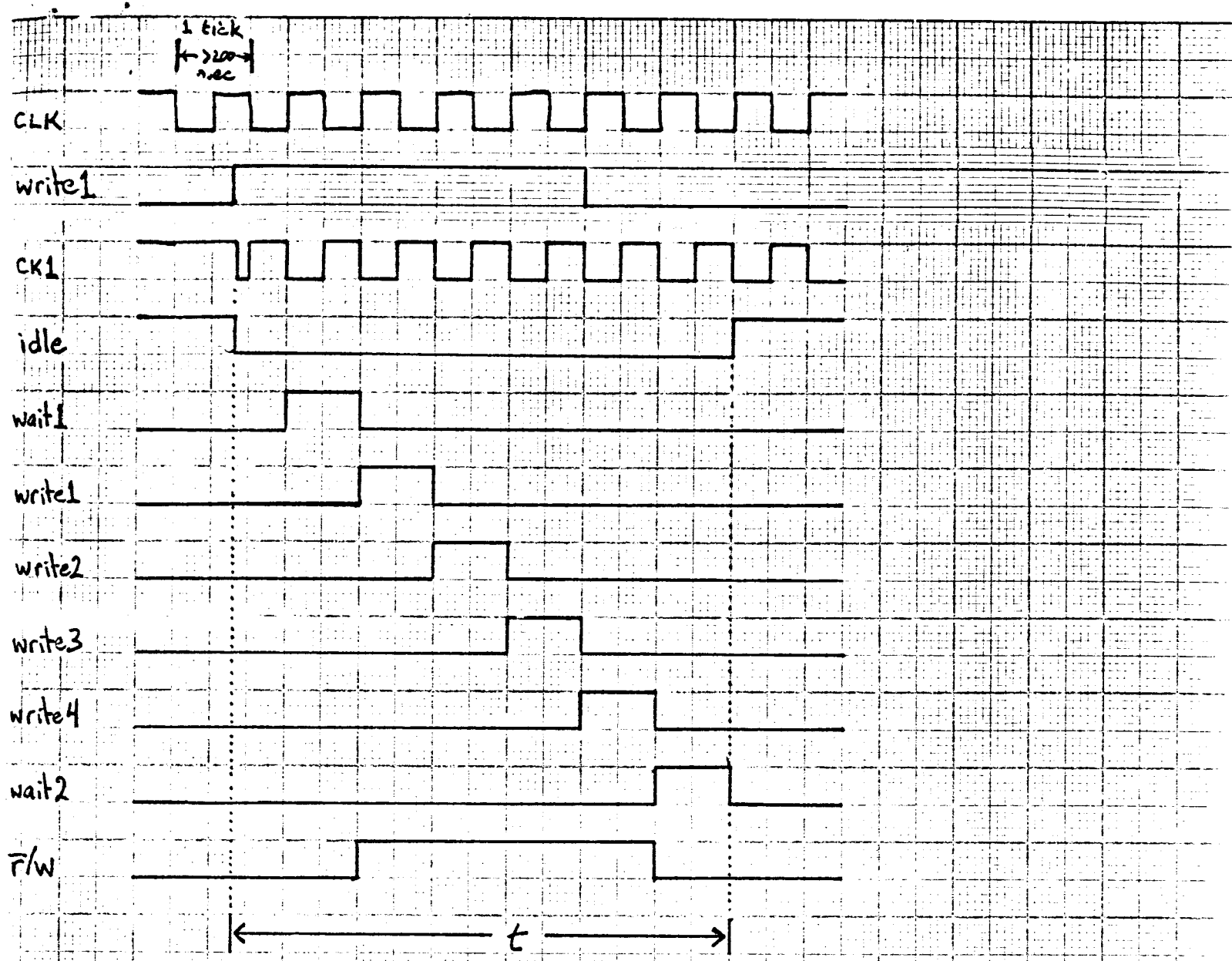

$7 \text{ ticks} < t < 8 \text{ ticks}$

Figure 13
Memory write cycle timing



 


Figure 14
 Φ_1, Φ_2 Timing

ALU instructions:

 

BRANCH instructions:

 

OP instructions:

 


Figure 15
Microcode Format

TYPES SN54181, SN54LS181, SN54S181, SN74181, SN74LS181, SN74S181 ARITHMETIC LOGIC UNITS/FUNCTION GENERATORS

description (continued)

ALU Signal Designations

The '181, 'LS181, and 'S181 can be used with the signal designations of either Figure 1 or Figure 2.

The logic functions and arithmetic operations obtained with signal designations as in Figure 1 are given in Table 1; those obtained with the signal designations of Figure 2 are given in Table 2.

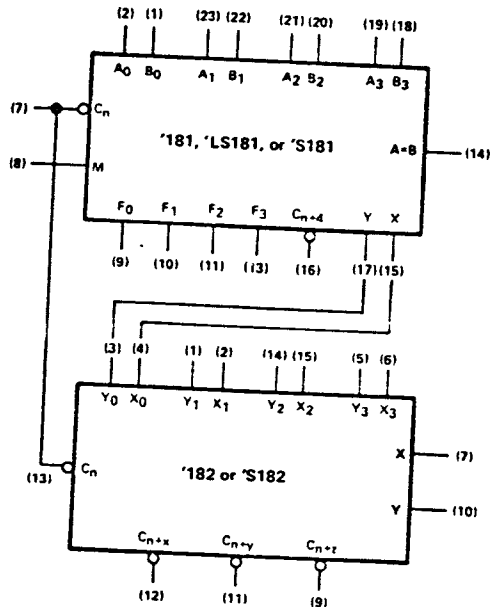


FIGURE 1
(FOR TABLE 1)

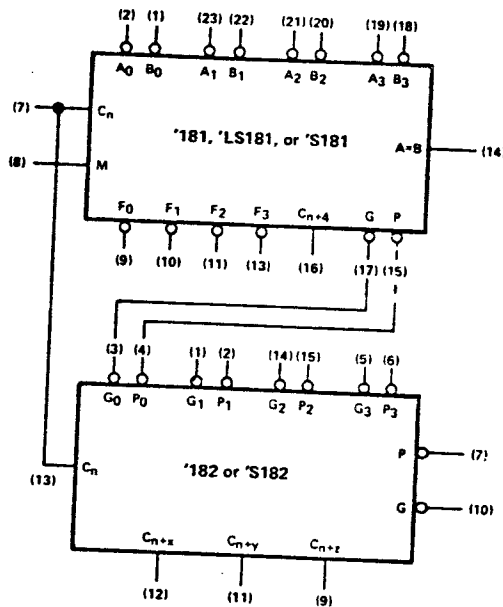


FIGURE 2
(FOR TABLE 2)

TABLE 1

SELECTION S3 S2 S1 S0	ACTIVE HIGH DATA		
	M = H LOGIC FUNCTIONS	M = L ARITHMETIC OPERATIONS	
		C _n = H (no carry)	C _n = L (with carry)
L L L L	F = \bar{A}	F = A	F = A PLUS 1
L L L H	F = $\bar{A} \oplus B$	F = A + B	F = (A + B) PLUS 1
L L H L	F = $\bar{A} \oplus B$	F = A + B	F = (A + B) PLUS 1
L L H H	F = 0	F = MINUS 1 (2's COMPL)	F = ZERO
L H L L	F = $\bar{A} \oplus B$	F = A PLUS AB	F = A PLUS AB PLUS 1
L H L H	F = \bar{B}	F = (A + B) PLUS AB	F = (A + B) PLUS AB PLUS 1
L H H L	F = $\bar{A} \oplus B$	F = A MINUS B MINUS 1	F = A MINUS B
L H H H	F = $\bar{A} \oplus B$	F = AB MINUS 1	F = AB
H L L L	F = $\bar{A} \oplus B$	F = A PLUS AB	F = A PLUS AB PLUS 1
H L L H	F = $\bar{A} \oplus B$	F = A PLUS B	F = A PLUS B PLUS 1
H L H L	F = B	F = (A + B) PLUS AB	F = (A + B) PLUS AB PLUS 1
H L H H	F = $\bar{A} \oplus B$	F = AB MINUS 1	F = AB
H H L L	F = 1	F = A PLUS A	F = A PLUS A PLUS 1
H H L H	F = $\bar{A} \oplus B$	F = (A + B) PLUS A	F = (A + B) PLUS A PLUS 1
H H H L	F = $\bar{A} \oplus B$	F = (A + B) PLUS A	F = (A + B) PLUS A PLUS 1
H H H H	F = A	F = A	F = A

*Each bit is shifted to the next more significant position.

TABLE 2

SELECTION S3 S2 S1 S0	ACTIVE LOW DATA		
	M = H LOGIC FUNCTIONS	M = L ARITHMETIC OPERATIONS	
		C _n = L (no carry)	C _n = H (with carry)
L L L L	F = \bar{A}	F = A MINUS 1	F = A
L L L H	F = $\bar{A} \oplus B$	F = AB MINUS 1	F = AB
L L H L	F = $\bar{A} \oplus B$	F = $\bar{A} \oplus B$ MINUS 1	F = $\bar{A} \oplus B$
L L H H	F = 1	F = MINUS 1 (2's COMPI)	F = ZERO
L H L L	F = $\bar{A} \oplus B$	F = A PLUS (A + B)	F = A PLUS (A + B) PLUS 1
L H L H	F = \bar{B}	F = AB PLUS (A + B)	F = AB PLUS (A + B) PLUS 1
L H H L	F = $\bar{A} \oplus B$	F = A MINUS B MINUS 1	F = A MINUS B
L H H H	F = $\bar{A} \oplus B$	F = A + B	F = (A + B) PLUS 1
H L L L	F = $\bar{A} \oplus B$	F = A PLUS (A + B)	F = A PLUS (A + B) PLUS 1
H L L H	F = $\bar{A} \oplus B$	F = A PLUS B	F = A PLUS B PLUS 1
H L H L	F = B	F = AB PLUS (A + B)	F = AB PLUS (A + B) PLUS 1
H L H H	F = $\bar{A} \oplus B$	F = A + B	F = (A + B) PLUS 1
H H L L	F = 0	F = A PLUS A	F = (A + B) PLUS 1
H H L H	F = $\bar{A} \oplus B$	F = AB PLUS A	F = AB PLUS A PLUS 1
H H H L	F = $\bar{A} \oplus B$	F = AB PLUS A	F = AB PLUS A PLUS 1
H H H H	F = A	F = A	F = A PLUS 1

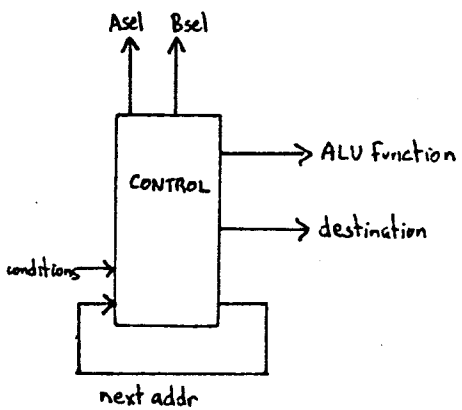
 


Figure 18
STUPID block diagram

DIGITAL SYSTEMS LAB

BACKPLANE LAYOUT

BOARD #	FUNCTION
MSI 151	CONTROL
500	
MSI 161	
LSI 1702	CLOCK
LSI 1702	
MSI 161	DISPATCH MUX
MSI 161	
MSI 122	ALU
MSI 157	
MSI 181	AMUX
MSI 181	
MSI 181	BMUX
MSI 153	
MSI 153	SWITCH REG
MSI 153	
MSI 153	PC
MSI 153	
MSI 153	
MSI 157	
MSI 157	
SWITCHES	
MSI 161	

1
RAIL

BOARD #	FUNCTION
574	MEMORY
574	
500	
600A	MBR
525	
LSI 2102	GROK
575	
575	MUX
575 529	
MSI 107	AC
MSI 153	
MSI 153	AC DISPLAY
MSI 161	
MSI 161	Random
MSI 161	
MSI 161	MAGIC MODE
MSI 161	
LIGHTS	MAR
574	
500	PC, MAR DISPLAY
SWITCH/LIGHTS	
MSI 161	
NUMBERS	

2
RAIL

BOARD #	FUNCTION
LITES (LED)	MICRO-INSTRUCTION DISPLAY
500	Random
574	2-phase clock gen
525	=0 detect
521	=0 detect
500	Random
UART	TTY OUT
TTY	Random
532	Gate delays

RAIL

7397

$$\begin{array}{r} 7397 \\ 647 \\ \hline 6750 \\ 429 \end{array}$$
 Figure 99
 7179

 


Figure 99a
STUPID display

; STUPID microcode

```

00 2802  gnorf:  bnss .+2          ; Magic mode?
01 0090          br test          ; Yes! Go load memory
02 2002  wait:  bnstart .        ; No. Wait for START
03 F7E8          pc<-swr         ; Start at addr in switches
04 0009          br inst

; Get next instruction and execute it:
05 2809  next:  bnss inst        ; Single stepping?
06 2008          bnstart .+2     ; Yes - make sure START is off
07 0006          br .-1         ; It wasn't
08 2008          bnstart .       ; Now wait for him to press it
09 B7C4  inst:  mar<-pc         ; Get the instruction
0A 4002          read
0B B008          pc<-pc+1        ; Get ready for next
0C 180C          bmr .          ; Now wait for the bloody thing
0D 6010          disp 10        ; Dispatch on op code
0E 000E          br .
0F 000F          br .          ; Bad news

10 00E0          br halt        ; OP 0 = HALT
11 0027          br add         ; OP 1 = ADD mem to AC
12 002C          br sub        ; OP 2 = SUBtract mem from AC
13 0031          br and        ; OP 3 = AND mem with AC
14 0036          br or         ; OP 4 = OR mem with AC
15 003B          br clr        ; OP 5 = CLear mem
16 0040          br isz        ; OP 6 = Inc mem, Skip if result=0
17 004B          br dsz        ; OP 7 = Dec mem, skip if result=0
18 0056          br load       ; OP 8 = LOAD AC from mem
19 005B          br store      ; OP 9 = STORE AC in mem
1A 001A          br .          ; OP A = HANG
1B 0060          br branch     ; OP B = Branch to mem
1C 0062          br bz         ; OP C = Branch if (AC)=0
1D 0065          br bn         ; OP D = Branch if (AC)<0
1E 0067          br bp         ; OP E = Branch if (AC)>0
1F 97E1          mwr<-ac       ; Op F = Special functions (like I/O)
20 9664          mar<-0
21 4001          write         ; Save AC in location 0
22 D590          ac<-shift(mbr) ; Shift left 4 bits
23 9590          ac<-shift(ac) ; to get the operation
24 9590          ac<-shift(ac)
25 9590          ac<-shift(ac)
26 006D          br patch     ; OOPS!

27 C7E4  add:   mar<-mbr
28 4002          read
29 1829          bmr .
2A 8530          ac<-ac+mbr
2B 0005          br next

2C C7E4  sub:   mar<-mbr
2D 4002          read

```

```

2E 182E      bmnr .
2F 80D0      ac<-ac-mbr
30 0005      br next

31 C7E4 and:  mar<-mbr
32 4002      read
33 1833      bmnr .
34 8770      ac<-ac&mbr
35 0005      br next

36 C7E4 or:   mar<-mbr
37 4002      read
38 1838      bmnr .
39 87D0      ac<-ac!mbr
3A 0005      br next

3B C7E4 clr:  mar<-mbr
3C 8661      mwr<-0
3D 4001      write
3E 183E      bmnr .
3F 0005      br next

40 C7E4 isz:  mar<-mbr
41 4002      read
42 1842      bmnr .
43 D001      mwr<-mbr+1
44 4003      write,read
45 1845      bmnr .
46 D7C1      mwr<-mbr!0      ; Compare
47 3849      b=0 .+2          ; Result=0?
48 0005      br next      ; Nope. skip the skip
49 B008      pc<-pc+1    ; Yes - skip next instr
4A 0005      br next

4B C7E4 dsz:  mar<-mbr
4C 4002      read
4D 184D      bmnr .
4E D5E1      mwr<-mbr-1
4F 4003      write,read
50 1850      bmnr .
51 D7C1      mwr<-mbr!0
52 3854      b=0 .+2
53 0005      br next
54 B008      pc<-pc+1
55 0005      br next

56 C7E4 load: mar<-mbr
57 4002      read
58 1858      bmnr .
59 D7F0      ac<-mbr
5A 0005      br next

```

```

5B C7E4 store: mar<-mbr
5C 97E1      mwr<-ac
5D 4001      write
5E 185E      bmnr .
5F 0005      br next

60 D7E8 branch: pc<-mbr
61 0005      br next          ; Simplicity personified

62 97D0 bz:      ac<-ac!0
63 3860      b=0 branch
64 0005      br next

65 3060 bn:      bac<0 branch
66 0005      br next

67 3005 bp:      bac<0 next          ; If <0 it can't be positive
68 97D0      ac<-ac!0              ; If = 0 it's not either
69 3805      b=0 next
6A D7E8      pc<-mbr              ; It's positive!!
6B 0005      br next
6C 006C      br .
6D 186D patch: bmnr .
6E 00CA      br pl                ; Go figger out what instr is
6F 006F      br .

; Dispatch table for OP F instructions
70 0080      br getbak            ; F0X = NOP
71 0085      br gchar             ; F1X = Get char from TTY
72 0088      br pchar             ; F2X = Type (AC) on TTY
73 00C7      br rswr              ; F3X = Read Switch register
74 0080      br getbak            ; F4X = NOP
75 0080      br getbak            ; F5X = NOP
76 0080      br getbak            ; F6X = NOP
77 0080      br getbak            ; F7X = NOP
78 0080      br getbak            ; F8X = NOP
79 0080      br getbak            ; F9X = NOP
7A 0080      br getbak            ; FAX = NOP
7B 0080      br getbak            ; FBX = NOP
7C 0080      br getbak            ; FCX = NOP
7D 0080      br getbak            ; FDX = NOP
7E 0080      br getbak            ; FEX = NOP
7F 0080      br getbak            ; FFX = NOP

80 9664 getbak: mar<-0          ; Get AC back from loc 0
81 4002      read
82 1882      bmnr .
83 D7F0      ac<-mbr
84 0005      br next

85 0885 gchar: bnchr .          ; Char in buffer?
86 9F50      ac<-tty            ; Yes. Read it in
87 0005      br next

```

```

88 9664 pchar: mar<-0 ; Get the char back
89 4002 read
8A 188A bmnr .
8B D7F0 ac<-mbr
8C 108C bnobe . ; Output buffer empty?
8D 97E2 tty<-ac ; Yes - send the char
8E 0005 br next ; Yipe!!!!
8F 008F br .

90 9670 test: ac<-0
91 97C8 pc<-ac!0 ; A little test to see if the machine
92 3894 b=0 .+2 ; maybe possibly might work
93 0093 br . ; It don't.
94 B7C4 mar<-pc!0
95 3897 b=0 .+2
96 0096 br . ; pc is broken
97 9661 mwr<-0
98 4001 write ; Location 0 = 0
99 1899 bmnr .
9A 4002 read
9B 189B bmnr . ; Hang here and memory is kaput
9C 87D0 ac<-ac!mbr
9D 38C5 b=0 gotcha ; Did we read back a 0?
9E 009E br . ; NO! memory is no good
9F 009F br .

; Dispatch table for simple dispatch test
A0 00B0 br ok ; Looks like disp might work
A1 00A1 br .
A2 00A2 br .
A3 00A3 br .
A4 00A4 br .
A5 00A5 br .
A6 00A6 br .
A7 00A7 br .
A8 00A8 br .
A9 00A9 br .
AA 00AA br .
AB 00AB br .
AC 00AC br .
AD 00AD br .
AE 00AE br .
AF 00AF br .

B0 9461 ok: mwr<- -1 ; Maybe the memory is stuck on zero
B1 4001 write
B2 18B2 bmnr .
B3 4002 read
B4 18B4 bmnr .
B5 D750 ac<-mbr
B6 30B8 bac<0 .+2 ; Is it negative?
B7 00B7 br . ; No. Something's broken
B8 9010 ac<-ac+1

```

```

B9 97D0      ac<-ac!0      ; Was it in fact -1?
BA 38BC      b=0 .+2      ; well...?
BB 00BB      br .      ; arrrrgh!
BC 9010      ac<-ac+1    ; Now try something with not all
BD 97E1      mwr<-ac     ; the nibbles the same
BE 4001      write
BF 18BF      bmnr .
C0 4002      read
C1 18C1      bmnr .
C2 D5F0      ac<-mbr-1
C3 38F0      b=0 exam    ; Looks maybe like it works
C4 00C4      br .

C5 60A0      gotcha: disp 40
C6 00C6      br .

C7 F7F0      rswr:      ac<-swr      ; Read switches
C8 0005      br next
C9 00C9      br .
CA 97E1      pl:        mwr<-ac
CB 9464      mar<- -1    ; Need a location to write thru
CC 4003      write,read  ; so we can get cpcode back into MBR
CD 18CD      bmnr .
CE 6070      disp 70
CF 00CF      br .

D0 2802      memlod:    bnss halt    ; Magic mode off?
D1 4800      lite      ; No - light the light
D2 20D0      bnstart .-2 ; and wait for 1 or the other
D3 B7C4      mar<-pc    ; Deposit
D4 F7E1      mwr<-swr
D5 4001      write
D6 B008      pc<-pc+1
D7 18D7      bmnr .
D8 20F1      bnstart displ ; /must unpress START
D9 00D8      br .-1
DA 00DA      br .
DB 00DB      br .
DC 00DC      br .
DD 00DD      br .
DE 00DE      br .
DF 00DF      br .

E0 2002      halt:      bnstart wait
E1 00E0      br .-1    ; On HALT, must unpress START
E2 00E2      br .
E3 00E3      br .
E4 00E4      br .
E5 00E5      br .
E6 00E6      br .
E7 00E7      br .
E8 00E8      br .
E9 00E9      br .

```



```

EA 00EA      br .
EB 00EB      br .
EC 00EC      br .
ED 00ED      br .
EE 00EE      br .
EF 00EF      br .

F0 F7E8      exam:  pc<-swr          ; Magic Mode: Examine loc in swr
F1 B7C4      displ: mar<-pc
F2 4002      read
F3 18F3      bmr .
F4 D750      ac<-mbr          ; Display it
F5 00D0      br memlod        ; and let him change it
F6 00F6      br .              ; if he wants to
F7 00F7      br .
F8 00F8      br .
F9 00F9      br .
FA 00FA      br .
FB 00FB      br .
FC 00FC      br .
FD 00FD      br .
FE 00FE      br .
FF 00FF      br .

```

addr	Cause?
02	START broken
0C	Mem hang on read
0E	DISPATCH doesn't do branch
0F	????????
1A	HANG instruction executed
29	Mem hang on read
2E	Mem hang on read
33	Mem hang on read
38	Mem hang on read
3E	Mem hang on write
42	Mem hang on read
45	Mem hang on simul write,read
4D	Mem hang on read
50	Mem hang on simul write,read
58	Mem hang on read
5E	Mem hang on write
6C	????????
6D	Mem hang on write
6F	????????
82	Mem hang on read
85	TTY in not raising DA
8A	Mem hang on read
8C	TTY out not raising TBE/
8F	????????
93	AC not loading or result=0 FF kaput
96	PC not loading properly
99	Mem hang on write
9B	Mem hang on read
9E	Val read from mem is not same as val written
9F	????????
A1-AF	DISPATCH or memory kaput
B2	Mem hang on write
B4	Mem hang on read
B7	Either read does not get written data or AC<0 is broken
BB	read data not same as written data (Mem stuck on zero?)
BF	Mem hang on write
C1	Mem hang on read
C4	Mem writes same thing to all 3 nibbles?
C6	DISPATCH broken
C9	????????

CF ?????????
D7 Mem hang on write
DA-DF ?????????
E2-EF ?????????
F3 mem hang on read
F6-FF ?????????

```

; STUPID demonstration program
; Accepts two BCD numbers (4 digits each)
; from the switches, typing them out
; on the TTY as they are read in. Then
; goes into operation mode, where the two
; numbers can be added, subtracted, anded or ored
; and the result printed in octal on the TTY.

```

```

; Start at location 9E. Antisocial people start
; at location 05

```

```

                .loc      5

05  587  gnorf:  clear    res1      ; Will hold 1st operand
06  588                clear    res2      ; 2nd operand
07  87E                load     four     ; 4 BCD digits per word
08  98B                store    count
09  98C                store    tnuoc

0A  F30  grok:   reads                ; read the ol' switches
0B  37B                and      hibit
0C  C0E                bz      igor      ; Make sure Hi order bit is off
0D  B0A                branch   grok      ; Otherwise must wait

0E  F30  igor:   reads                ; Get the value
0F  989                store    s
10  37B                and      hibit      ; High bit=1 => take it
11  C0E                bz      igor
12  889                load     s          ; Get num back
13  382                and      f          ; Mask to digit
14  989                store    s          ; s has BCD digit
15  181                add     zero     ; Type it out
16  F20                pchar
17  887                load     res1      ; Old result
18  187                add     res1      ; old*2
19  98A                store    temp
1A  18A                add     temp      ; old*4
1B  987                store    res1
1C  187                add     res1      ; old*8
1D  18A                add     temp      ; old*10
1E  189                add     s          ; old*10+new
1F  987                store    res1
20  78B                dsz     count     ; Got 4 digits?
21  B0A                branch   grok      ; Not yet

22  87F                load     cr
23  F20                pchar                ; Ker
24  880                load     lf
25  F20                pchar                ; chink
26  F30  korg:   reads
27  37B                and      hibit
28  C2A                bz      rogi      ; Wait for it to go low again
29  B26                branch   korg

```

```

2A F30   rogi:   reads
2B 989           store      s
2C 37B           and        hibit
2D C2A           bz         rogi
2E 889           load       s
2F 382           and        f
30 989           store      s
31 181           add        zero
32 F20           pchar
33 888           load       res2
34 188           add        res2
35 98A           store      temp
36 18A           add        temp
37 988           store      res2
38 188           add        res2
39 18A           add        temp
3A 189           add        s
3B 988           store      res2
3C 78C           dsz        tnouc
3D B26           branch    korg
3E 87F   crlf:  load       cr
3F F20           pchar
40 292           load       lf
41 F20           pchar

42 F30   loop:   reads
43 37B           and        hibit
44 D42           bn         loop
                                ; Hey, I don't need this instr!
                                ; Because it's negative anyway

45 F30   pool:   reads
46 989           store      s
47 37B           and        hibit
48 C45           bz         pool

49 889           load       s
4A 383           and        sum
4B E56           bp         addem
4C 889           load       s
4D 384           and        diff
4E E59           bp         subem
4F 889           load       s
50 385           and        .and
51 E5C           bp         andem
52 889           load       s
53 386           and        .or
54 E5F           bp         orem
55 000           halt

                                ; Look for operation now
                                ; He wanna add?
                                ; Yup.
                                ; Subtract?
                                ; and?
                                ; or?
                                ; None of the above. Quit.

56 887   addem:  load       res1
57 188           add        res2
58 B62           branch    type
                                ; Go type out the result

```

```

9 887 subem: load res1
A 288 sub res2
B B62 branch type

C 887 andem: load res1
D 388 and res2
E B62 branch type

F 887 orem: load res1
0 488 or res2
1 B62 branch type

2 98A type: store temp ; Save result
3 87E load four ; Four octal digits per word
4 98C store tnuoc

5 87D there: load three ; 3 bits per octal digit
6 98B store count
7 58D clear digit
8 88A here: load temp ; Get word back
9 37B and hibit
A C6C bz ; 0 or 1?
B 87C load one ; 1 - make it 1 instead of 1B11
C 98E skip: store xxx ; Save the bit
D 88A load temp
E 18A add temp
F 98A store temp ; Shift result word
0 88D load digit ; Running sum...
1 18D add digit ; *2
2 18E add xxx ; + bit
3 98D store digit ; And that's the new one...
4 78B dsz count ; Got a whole octal digit yet?
5 B68 branch here ; Nope. Keep going

6 181 add zero ; ASCII-ize it
7 F20 pchar ; Type the digit
8 78C dsz tnuoc ; Finished?
9 B65 branch there ; Not yet
A B3E branch crlf ; Yes. Go get another op

B 800 hibit: 800 ; Most signif bit
C 001 one: 1 ; Yup.
D 003 three: 3
E 004 four: 4
F 00D cr: D ; Carriage return
0 00A lf: B ; Line feed
1 030 zero: 30 ; ASCII "0"
2 00F f: F ; Low order 4 bit mask
3 001 sum: 1 ; Bit which means "add"
4 002 diff: 2 ; "subtract"
5 004 .and: 4 ; "and"
6 008 .or: 8 ; "or"
7 000 res1: 0

```

```

38 000 res2: 0
39 000 s: 0
3A 000 temp: 0
3B 000 count: 0
3C 000 tnuoc: 0
3D 000 digit: 0
3E 000 xxx: 0

.loc 9E

9E 8A8 start: load lenth
9F 98B store count
A0 8A9 load kludge
A1 9A2 store inst
A2 8AA inst: load msg
A3 F20 pchar ; Type out something
A4 6A2 isz inst ; Next char...
A5 78B dsz count ; Done?
A6 BA2 br inst ; Notchet
A7 B05 br gnorf

A8 00B lenth: B ; 11 chars in mess
A9 8AA kludge: load msg ; typer modifies inst...
AA 048 msg: "H
AB 049 "I
AC 020 "
AD 054 "T
AE 048 "H
AF 045 "E
B0 052 "R
B1 045 "E
B2 00D D
B3 00B B
B4 00B B

.end

```