

## Nodal Analysis applied to Active circuits

Active circuits can be solved by many different techniques. Using those techniques often require dividing a circuit into multiple separate blocks of forward and feedback functions. Sometimes it is a very difficult task to determine forward and feedback paths of a particular linear active circuit. Any linear circuit can be solved as a combination of linear equations. These equations can be written around voltage nodes. Nodal analysis is widely used to analyze passive networks. The following figure shows a basic resistive network.

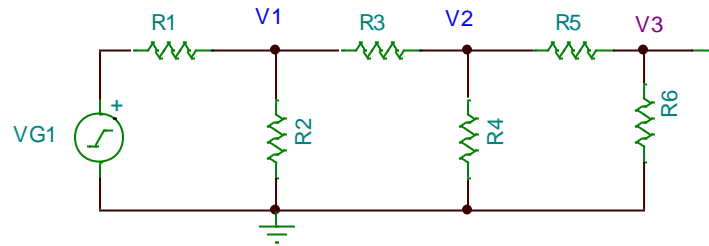


Figure 1

The circuit has three nodes, which can be described in three linear equations.

$$V1 \left( \frac{1}{R1} + \frac{1}{R2} + \frac{1}{R3} \right) - \frac{1}{R1} VG1 - \frac{1}{R3} V2 = 0$$

$$V2 \left( \frac{1}{R3} + \frac{1}{R4} + \frac{1}{R5} \right) - \frac{1}{R3} V1 - \frac{1}{R5} V3 = 0$$

$$V3 \left( \frac{1}{R5} + \frac{1}{R6} \right) - \frac{1}{R5} V2 = 0$$

Solution for voltages V1, V2, and V3 can be found using linear algebra techniques.

A basic nodal analysis can be easily applied to any linear active circuit. For example lets take a look at a second order low-pass filter.

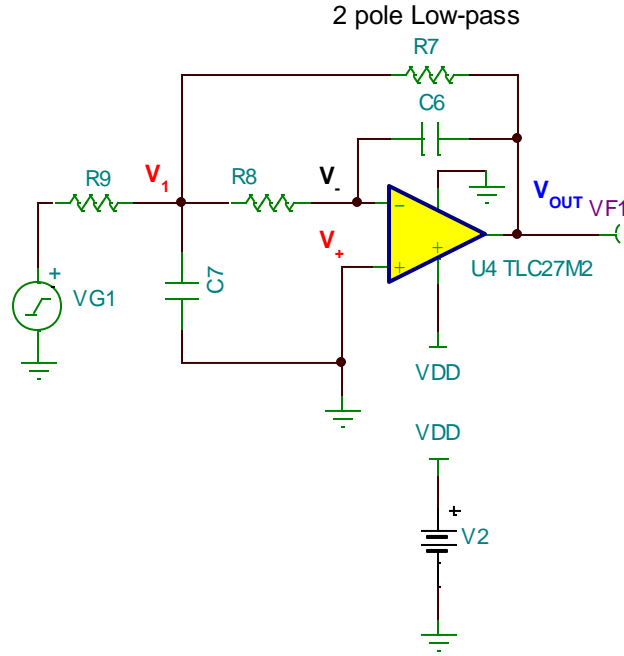


Figure 2

Using nodal analysis the following can be obtained at nodes V1 and V<sub>-</sub>:

$$V1 \left( \frac{1}{R9} + \frac{1}{R8} + \frac{1}{R7} + sC7 \right) - \frac{1}{R9} VG1 - \frac{1}{R7} V_{OUT} - \frac{1}{R8} V_- = 0 \quad (1)$$

$$V_- \left( \frac{1}{R8} + sC6 \right) - sC6 V_{OUT} - \frac{1}{R8} V1 = 0 \quad (2)$$

Assuming ideal operational amplifier, the following is true:

$$V_- = V_+ = 0$$

In equation (1) the term that contains  $1/R8 V_-$  is zero.

$$V1 \left( \frac{1}{R9} + \frac{1}{R8} + \frac{1}{R7} + sC7 \right) - \frac{1}{R9} VG1 - \frac{1}{R7} V_{OUT} = 0 \quad (3)$$

In equation (2) the term that contains  $V_- \left( \frac{1}{R8} + sC6 \right)$  is also zero.

$$- sC6 V_{OUT} - \frac{1}{R8} V1 = 0 \quad (4)$$

The first term in equation (3) can be presented as follows:

$$V1 \left( \frac{1}{R9} + \frac{1}{R8} + \frac{1}{R7} + sC7 \right) = V1 \frac{R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7}{R9 R8 R7} \quad (5)$$

Substitute (5) into equation (1), we will get:

$$V1 \frac{R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7}{R9 R8 R7} - \frac{1}{R9} VG1 - \frac{1}{R7} V_{OUT} = 0 \quad (6)$$

From equation (4) we can determine  $V_{OUT}$ .

$$V_{OUT} = - \frac{1}{sC6 R8} V1 \quad (7)$$

Solving for  $V1$  in equation (6).

$$V1 = \frac{R9 R8 R7}{R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7} \left( \frac{1}{R9} VG1 + \frac{1}{R7} V_{OUT} \right) \quad (8)$$

Substituting equation (8) into equation (7) we will get.

$$V_{OUT} = - \frac{1}{sC6 R8} \frac{R9 R8 R7}{R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7} \left( \frac{1}{R9} VG1 + \frac{1}{R7} V_{OUT} \right) \quad (9)$$

Simplifying

$$\begin{aligned} V_{OUT} \left( 1 + \frac{R9}{sC6(R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7)} \right) \\ = - \frac{R7}{sC6(R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7)} VG1 \\ V_{OUT} \left( \frac{sC6(R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7) + R9}{sC6(R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7)} \right) \\ = - \frac{R7}{sC6(R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7)} VG1 \\ V_{OUT} = - \frac{R7}{sC6(R7 R8 + R7 R9 + R8 R9 + R9 R8 R7 sC7) + R9} VG1 \quad (10) \end{aligned}$$

The above equation can be rewritten as:

$$\begin{aligned} V_{OUT} = - \frac{\frac{1}{R9 R8 C7 C6}}{s^2 + s \frac{C6 R7 R8 + C6 R7 R9 + C6 R8 R9}{R9 R8 R7 C7 C6} + \frac{1}{R8 R7 C7 C6}} VG1 \\ V_{OUT} = - \frac{\frac{R7}{R8}}{s^2 R8 R7 C7 C6 + s \frac{C6 (R7 R8 + R7 R9 + R8 R9)}{R9} + 1} VG1 \end{aligned}$$

Where gain of the circuit is:  $A_0 = -\frac{R7}{R8}$

$$a_1 = \frac{C6 (R7 R8 + R7 R9 + R8 R9)}{R9}$$

$$b_1 = R8 R7 C7 C6$$

$$\omega = \frac{1}{\sqrt{R_8 R_7 C_7 C_6}}$$

Conclusion: Nodal analysis can be used on any type of linear circuit. Circuit nodes can be easily identified from a circuit diagram and a circuit solution becomes a straight forward mathematical manipulation.